

國立成功大學

111學年度碩士班招生考試試題

編 號： 41

系 所： 光電科學與工程學系

科 目： 電子學

日 期： 0220

節 次： 第 1 節

備 註： 不可使用計算機

---

※ 考生請注意：本試題不可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. A reverse-biased photodiode is specified to have a dark current of 100 pA and a responsivity of 0.5 A/W. It is connected to the transresistance amplifier shown in Fig. 1. Assume op amp is ideal. (20%)
  - (a) Please show five characteristics of ideal op amp. (10%)
  - (b) What is the output voltage  $v_o$  with 10  $\mu$ W of light incident on the photodiode? (10%)

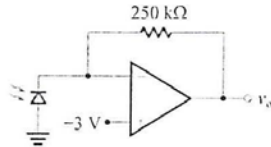


Fig. 1

2. For the circuit shown in Fig. 2, EBJ operated at 0.7 V for  $Q_1$  and  $Q_2$ , find  $V_1$ ,  $V_2$ , and  $V_3$ . (15%)

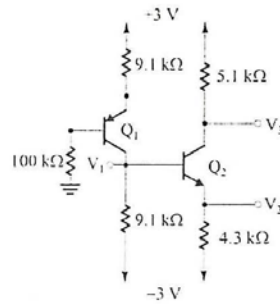


Fig. 2

3. In the circuit of Fig. 3, transistors  $Q_1$  and  $Q_2$  have  $V_t=0.7$  V,  $(W/L)_1=1.5(W/L)_2=20$ , and the process transconductance parameter  $k_n'=125 \mu\text{A}/\text{V}^2$ . Find  $V_1$ ,  $V_2$ , and  $V_3$ . (15%)

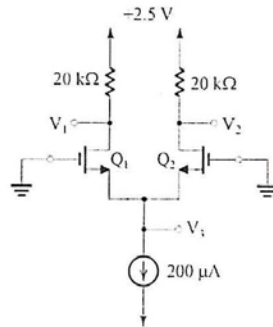


Fig. 3

4. The MOSFET (with aspect ratio of 10) in the amplifier circuit (Fig. 4) has threshold voltage ( $V_t$ ) of 0.4 V, the process transconductance parameter ( $k_n'$ ) of  $0.5 \text{ mA/V}^2$ , and the associated value of  $\lambda$  of  $0.02 \text{ V}^{-1}$ . The signal  $V_{sig}$  has a zero average. (25%)
- (a) It is required to bias the transistor to operate at an overdrive voltage  $V_{ov} = 0.1 \text{ V}$ . What must the dc voltage at the drain be? Calculate the dc drain current  $I_D$  taking into account  $\lambda$ . Now, what value must the drain resistance  $R_D$  have? ( $3 \times 3\% = 9\%$ )
- (b) Calculate the values of transconductance ( $g_m$ ) and output resistance ( $r_o$ ) at the bias point established in (a) ( $2 \times 3\% = 6\%$ )
- (c) Derive the expression for the voltage gain ( $V_o/V_{sig}$ ) using the small signal equivalent circuit of the amplifier. And find the value of the gain by using the  $r_o \sim 2 \text{ M}\Omega$ . (10%)

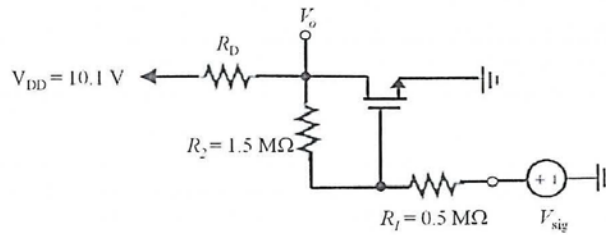


Fig. 4

5. The circuit of Fig. 5 shows a differential amplifier. (15%)
- (a) Find the differential half-circuit for the amplifier and use it to derive an expression for the differential gain  $A_d = v_{od}/v_{id}$  in terms of  $g_m$ ,  $R_D$ , and  $R_S$ . Neglect the early effect. (8%)
- (b) The resistance  $R_S$  in the circuit can be implemented by using a MOSFET ( $Q_3$ ) operated in the triode region. Here  $Q_3$  implements  $R_S$ , with the value of  $R_S$  determined by the gate voltage  $v_{G3}$  of  $Q_3$ . Consider the case  $v_{G1} = +v_{id}/2$  and  $v_{G2} = -v_{id}/2$ , where  $v_{id}$  is a small signal. Assume that  $Q_3$  now conducts current and operates in the triode region with a small  $v_{DS}$ . What resistance  $r_{DS}$  does it have, expressed in terms of the overdrive voltage  $V_{ov3}$  at which it is operating? This is the resistance  $R_S$ . Now if all three transistors have the same aspect ratio  $W/L$ , express  $R_S$  in terms of  $V_{ov}$ ,  $V_{ov3}$ , and  $g_{m1,2}$ . (7%)

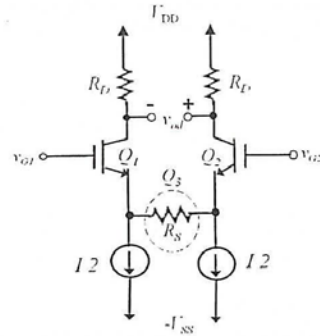


Fig. 5

6. The transistors in the circuit (Fig. 6) have  $\beta = 100$  and  $V_A = 50$  V. What is the effect of the increasing the bias currents by a factor of 10 on  $R_{in}$  and the overall voltage gain  $G_v$ ? (10%)

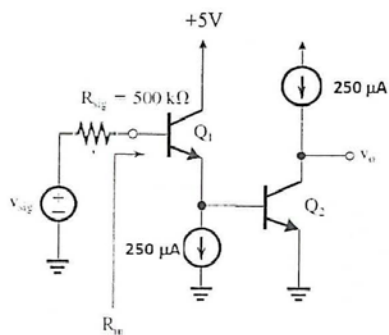


Fig. 6