 


科目：邏輯設計

系所組：電機工程學系丁組

1. Draw the logic circuit of a four-to-one-line multiplexer. (5%)
2. Simplify the following Boolean expression using **algebraic method**:  
 $A'B(D'+C'D) + B(A+A'CD) + ABEF$ . (5%)
3. Use four variables map to simplify the following Boolean function  $F$ , together with the don't-care  $d$ . Draw the logic diagram using two-level forms (a) AND-NOR (b) NOR-NOR; (c) NAND-NAND; (d) NOR-OR. (12%) (**Must not attach any inverter at the output**)  
 $F(A, B, C, D) = \sum m(0, 3, 4, 8, 10, 11)$ ,  $d(A, B, C, D) = \sum m(1, 2, 6)$
4. (a) How many  $32K \times 8$  RAM chips are needed to provide a memory capacity of 512K bytes? (b) How many lines of the address must be used to access 512K bytes? (c) How many of these lines are connected to the address inputs of all chips? (d) Specify the size of the address decoder needed in the design. (10%)
5. Consider the waveforms of a clock and of an input data signal as shown in Fig. 1. Connect them to (a) a positive level triggered D-latch (b) a positive edge triggered D flip-flop and (c) a negative edge triggered T flip-flop. Draw the output's (Q) waveform, assuming that the initial value of Q is 0. (**clock and input data 波形也要畫在答案紙上**) (6%)



6. Design a counter with the following repeated binary sequence: 0, 1, 4, 6, 5 using three (1) D flip-flops and (2) JK flip-flops. (15%)
7. A Moore sequential circuit has one input X and one output Y. The output  $Y=1$  iff the total number of 1's received is odd and divisible by 3, otherwise  $Y=0$ . (Note that 3, 9, 15 is odd and divisible by 3) (a) Draw the state diagram; (b) Write a behavioral HDL model (Verilog or VHDL) of the machine. (5%, 9%)
8. Assume X being a 3-bit unsigned number. Design a modular squarer circuit that generates  $X^2 \bmod 5$ . (e.g.  $X=4, X^2 \bmod 5 = 1$  and  $X=2, X^2 \bmod 5 = 4$ ) (10%)
9. Explain why the registered outputs are generally used in Mealy machine? (5%)
10. Briefly explain the following technical terms (18%)  
(1) static 1-hazard (2) hold time (3) ring counter (4) carry select adder (5) carry save adder (6) essential implicant.

※ 注意：1. 考生須在「彌封答案卷」上作答。

2. 本試題紙空白部份可當稿紙使用。

3. 考生於作答時可否使用計算機、法典、字典或其他資料或工具，以簡章之規定為準。