

科目：電子學

系所組：電機工程學系乙、丁組

1. For the circuit in Fig.1, assuming the amplifier is ideal:

- (1) Find the transfer function $T(s)=V_o(s)/V_i(s)$ in terms of $C_1, C_2,$ and $R.$ (8%)
- (2) For $C_1=C_2=0.5\mu\text{F}$ and $R=100\text{k}\Omega,$ find the location of the pole(s) and zero(s), and sketch Bode plots for the magnitude response and the phase response. (12%)

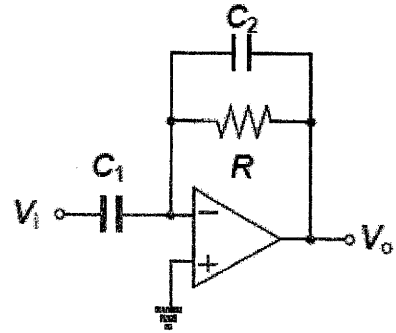


Fig. 1.

2. In Fig. 2, for the emitter follower biased at $I_C=1\text{mA}$ and having $r_x=100\Omega, r_o=100\text{k}\Omega, R_{sig}=R_L=1\text{k}\Omega, \beta=100, C_\mu=2\text{pF},$ and $f_T=400\text{MHz}:$

- (1) Find low-frequency gain. (10%)
- (2) Find the $f_z, R_{\mu s}, R_{\tau s}$ and $f_H.$ (10%)

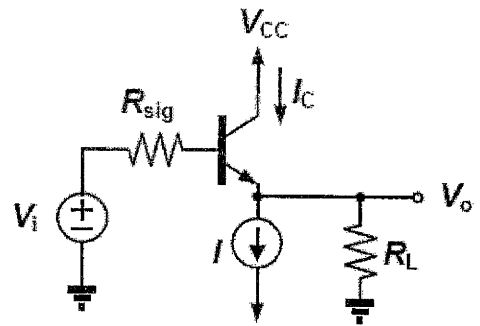


Fig. 2.

3. For the circuit in Fig.3, $I_D=1\text{mA}, R_1=1\text{M}\Omega, R_2=4\text{M}\Omega,$ and $V_{GS}=0.8\text{V}.$ The MOSFET has $V_t=0.6\text{V}.$ When channel length modulation, and parasitic are neglected,

- (1) What is the feedback type of this circuit in terms of series and shunt? (2%)
- (2) Find the feedback factor (β). (3%)
- (3) Find voltage gain V_o/V_i by feedback analysis. (10%)
- (4) Find input resistance (R_i) and output resistance (R_o). (5%)

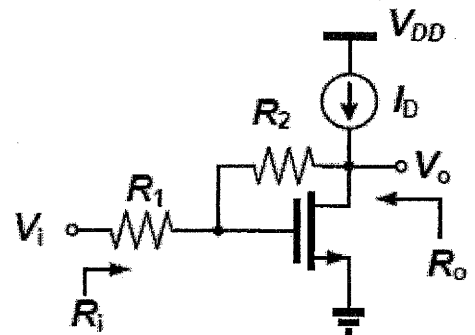


Fig. 3.

※ 注意：1.考生須在「彌封答案卷」上作答。
 2.本試題紙空白部份可當稿紙使用。
 3.考生於作答時可否使用計算機、法典、字典或其他資料或工具，以簡章之規定為準。

科目：電子學

系所組：電機工程學系乙、丁組

4. For circuits in Fig. 4, all transistors operate at saturation region and their corresponding transconductance of M_x is denoted as g_{m_x} . As the transistors are symmetric, and the channel length modulation, the body effect, parasitic are neglected,
- (1) Find the voltage gain of Fig. 4(a). (10%)
 - (2) Find the voltage gain of Fig. 4(b). (10%)

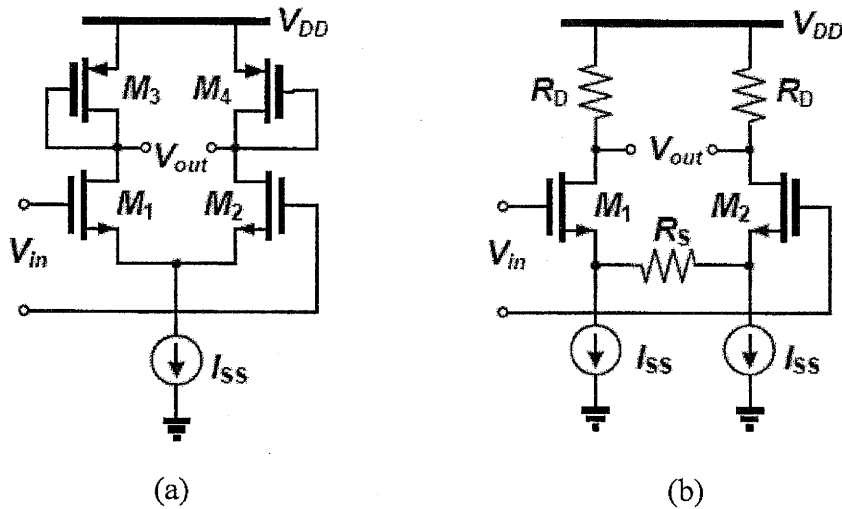


Fig. 4

5. Consider the circuit shown in Fig. 5(a)
- (1) If $Z_1 \sim Z_5$ represent general impedances and the two op amps are ideal, find the impedance (Z_{in}) from V_t to the ground. (10%)
 - (2) Derive the transfer function of Fig. 5(b) and determine the type of this filter. After that, find out the design of $Z_1 \sim Z_5$ with resistors and capacitors to replace the inductor. (10%)

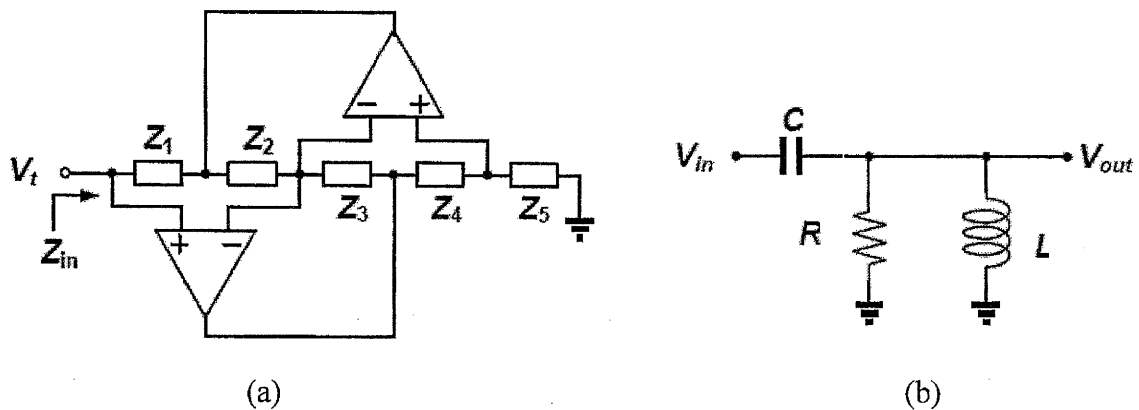


Fig. 5

※ 注意：1. 考生須在「彌封答案卷」上作答。
 2. 本試題紙空白部份可當稿紙使用。
 3. 考生於作答時可否使用計算機、法典、字典或其他資料或工具，以簡章之規定為準。