

國立成功大學

112學年度碩士班招生考試試題

編 號： 181、192、199

系 所：電機工程學系
電腦與通信工程研究所
電機資訊學院-微電、奈米聯招

科 目： 電子學

日 期： 0206

節 次： 第 1 節

備 註： 可使用計算機

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. (選擇題，每小題 5 分) Please choose the most appropriate answer for the following questions:

(1) The Bode Plot for an open loop gain $A(f)$ of an amplifier is shown in Fig. 1a. The amplifier is used with negative feedback and its DC closed-loop gain is 1,000. What is the gain margin of this amplifier with feedback?

- (a) 0 dB, (b) 20 dB, (c) 40 dB, (d) 60 dB.

(2) Follow (1), what is the phase margin of this amplifier with feedback.

- (a) -60° , (b) 45° , (c) 60° , (d) 135° .

(3) What is the value of the low-frequency power-supply rejection ratio with respect to V_{DD} ($PSRR^+ \equiv A_d / A^+$) for a well-matched two stage CMOS op amp shown in Fig. 1b, where g_m and r_o is the transconductance and output resistance of a MOSFET, respectively?

- (a) 0, (b) $\approx g_m r_o$, (c) $\approx (g_m r_o)^2$, (d) ∞ .

(4) Follow (3), what is the value of the low-frequency power-supply rejection ratio with respect to V_{SS} ($PSRR^- \equiv A_d / A^-$)?

- (a) 0, (b) $\approx g_m r_o$, (c) $\approx (g_m r_o)^2$, (d) ∞ .

(5) Which of the following properties is wrong while applying negative feedback to an open-loop amplifier?

- (a) Extends the 3db bandwidth
 (b) Improves gain stability
 (c) Increases gain-bandwidth product
 (d) Reduces nonlinear distortion

(6) For enhancing the high-frequency performance (such as slew-rate and unit-gain frequency) of a two-stage CMOS op amp, we should?

- (a) use smaller L for transistors, and operate transistors at larger overdrive voltage,
 (b) use smaller L for transistors, and operate transistors at smaller overdrive voltage,
 (c) use larger L for transistors, and operate transistors at larger overdrive voltage,
 (d) use larger L for transistors, and operate transistors at smaller overdrive voltage,

(7) What is the equivalent impedance of a LC resonator when the inductor (with inductance L) and capacitor (with capacitance C) are connected in series and resonate at a frequency of $\omega = 1/\sqrt{LC}$?

- (a) 0, (b) C/L , (c) L/C , (d) ∞ .

(8) The response of a second-order low-pass filter will be maximally flat for a Q factor equal to

- (a) $\sqrt{2}$, (b) 1, (c) $1/\sqrt{2}$, (d) 1/2.

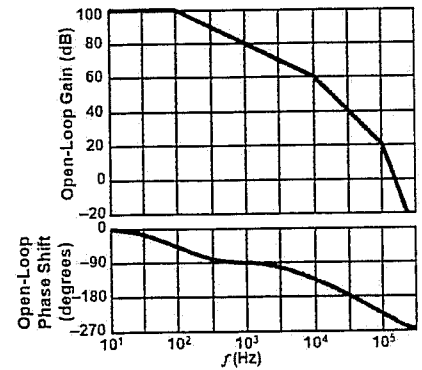


Fig. 1a

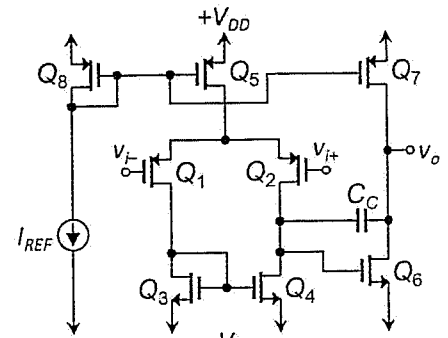


Fig. 1b

(9) Fig. 1c shows the output response of a single-time-constant (STC) low-pass circuit to a 10-V step input. Please find the time taken, in terms of the time constant τ , for the output to reach 9.9 V.

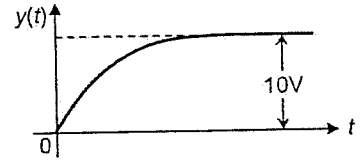


Fig. 1c

- (a) 0.69τ , (b) 2.2τ , (c) 3.3τ , (d) 4.6τ .

(10) What is the output resistance (R_{out}) of the Wilson current mirror shown in Fig. 1d, where g_{m1} and r_{o1} is the transconductance and output resistance of the MOSFET Q_1 , respectively?

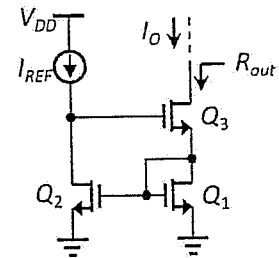


Fig. 1d

- (a) $r_{o3} + r_{o1}$,
 (b) $r_{o3} + (1/g_{m1})$,
 (c) $r_{o3} + g_{m3}r_{o3}(1/g_{m1})$,
 (d) $r_{o3} + g_{m3}r_{o3}(r_{o2})$

2. Fig. 2 considers the use of an op amp with unity-gain frequency of 20 MHz ($f_t = 20$ MHz), slew rate of $10 \text{ V}/\mu\text{s}$ ($SR = 10 \text{ V}/\mu\text{s}$), and $V_{omax} = 10\text{V}$ in the design of a noninverting amplifier with a nominal gain of 10. Assume $V_{in} = V_i \sin 2\pi ft$.

- (a) If $V_i = 0.5 \text{ V}$, what is the maximum frequency (f_{max}) before the output distorts? (4%)
 (b) If $f = 200 \text{ kHz}$, what is the maximum value of V_i (V_{imax}) before the output distorts? (4%)
 (c) If $V_i = 0.5 \text{ mV}$, what is the useful frequency range of operation (f_{3dB})? (4%)
 (d) If $f = 50\text{kHz}$, what is the useful input voltage range (v_i)? (4%)

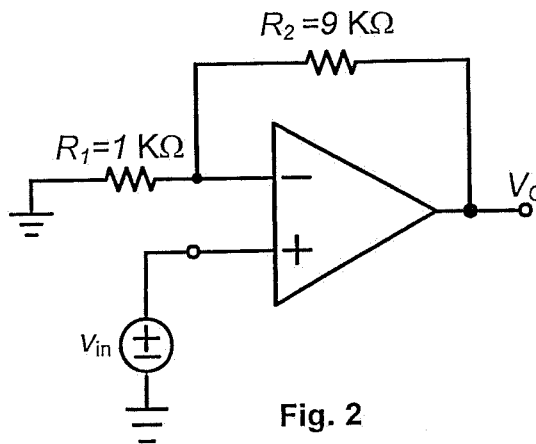


Fig. 2

3. The feedback amplifier of Fig. 3 consists of a common-gate amplifier formed by Q_1 and R_D , and a feedback circuit formed by the capacitive divider (C_1 and C_2) and the common-source transistor Q_f . Neglect r_o and the loading effect of C_1 and C_2 on the basic amplifier. Assume $g_m = 5 \text{ mA}/\text{V}$, $R_D = 10 \text{ k}\Omega$, $C_1 = 0.9 \text{ pF}$ and $C_2 = 0.1 \text{ pF}$, and $g_{mf} = 2 \text{ mA}/\text{V}$.

- (a) Find the voltage gain $A_f = V_o/I_s$ (4%)
 (b) Find the input resistance (R_{in}) and output resistance (R_{out}) (10%)

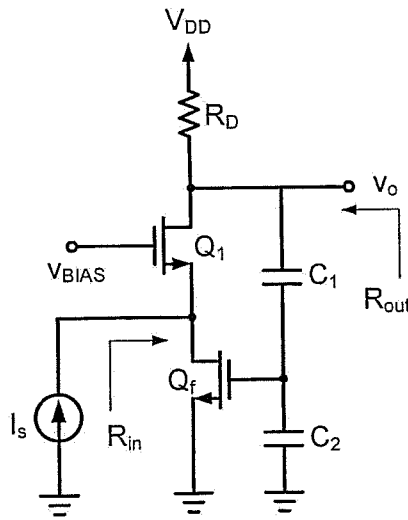


Fig. 3

4. The MOSFET in the circuit of Fig. 4 has threshold voltage $V_{tn} = 0.8 \text{ V}$, $k_n = \mu_n C_{ox}(W/L) = 5 \text{ mA/V}^2$, $R_G = 10 \text{ M}\Omega$, and Early voltage $V_A = 40 \text{ V}$
- Find the values of R_S and R_D , so that $I_D = 0.4 \text{ mA}$, the largest possible value for R_D is used while a maximum signal swing at the drain of $\pm 0.8 \text{ V}$ is possible. Neglect the Early effect. (4%)
 - Find the value of transconductance (g_m) and output resistance (r_o) of Q_1 at the bias point. (4%)
 - If the terminal Z is grounded, terminal X is connected to a signal source having a resistance of $1 \text{ M}\Omega$, and terminal Y is connected to a load resistance of $10 \text{ k}\Omega$, find the voltage gain from signal source to load. (4%)
 - If terminal Y is grounded, find the voltage gain from X to Z with Z open-circuited. What is the output resistance of the source follower? (4%)
 - If terminal X is grounded and terminal Z is connected to a current source delivering a signal current of $50 \mu\text{A}$, and having a resistance of $100 \text{ k}\Omega$, find the voltage signal that can be measured at Y. For simplicity, neglect the effect of r_o . (4%)

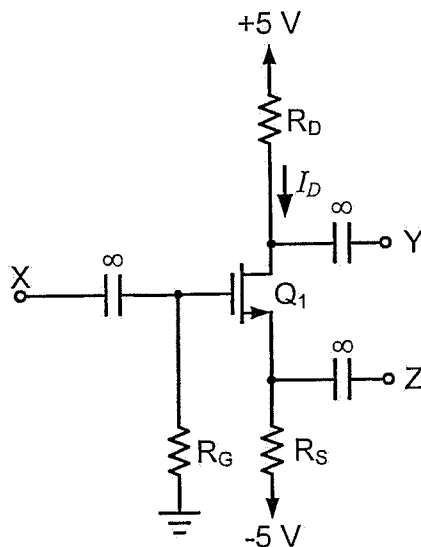


Fig. 4