

國立成功大學

112學年度碩士班招生考試試題

編 號：124

系 所：工程科學系


科 目：電子電路

日 期：0207


節 次：第 1 節

備 註：可使用計算機

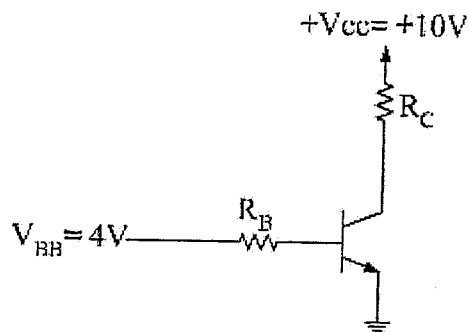
- ※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。
1. If β is 100 and I_{BQ} is $12\mu A$ and V_{CEQ} is 5V, what are the collector resistance (5%), base resistance (5%) and collector current (5%) ?



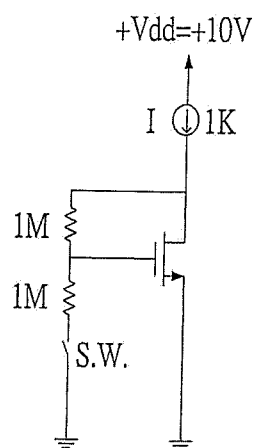2. It is known that when the switch (S.W) is opened (OPEN), $I = 6.5mA$, when the switch is shorted (CLOSE), $I = 4mA$, $V_t = 1.18V$, try to find EMOS
- (1) K_n coefficient? (10%)
 - (2) What is the role of the fixed power supply method added to this circuit? (10%)



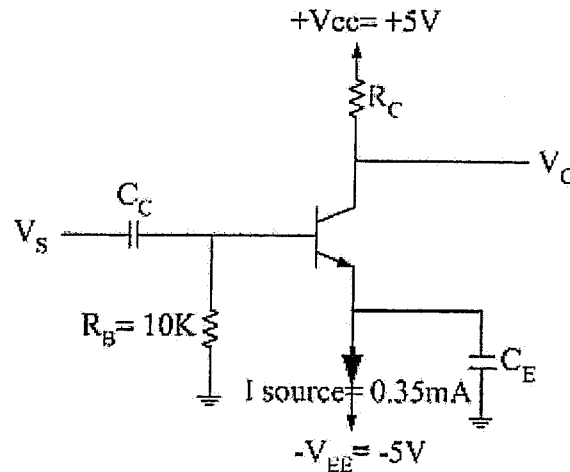3. If β is 100 and Early voltage (V_A) is 100V, please find (20%)
- the DC voltage at the base (V_B) and the emitter (V_E); (5%)
 - if V_{CEQ} is 3.5V, find the value of the required collector resistance? (5%)
 - If the bypass and coupling capacitor are shorted, find the small signal voltage gain $A_V=V_O/V_S$ (5%)
 - If there is a 500Ω resistor in series with V_S , redo the problem in (c)? (5%)



4. If β is known to be 180 and the output resistance is ∞ . (20%)
- the values of I_{BQ} , I_{CQ} and V_{CEQ} (5%)
 - the small signal g_m/r_n (5%)
 - the small signal voltage gain $A_V=V_O/V_S$? (10%)

