

國立中正大學
112 學年度碩士班招生考試
試題

[第 2 節]

科目名稱	電子學
系所組別	電機工程學系- 電磁晶片組 計算機工程組 晶片系統組

— 作答注意事項 —

※作答前請先核對「試題」、「試卷」與「准考證」之系所組別、科目名稱是否相符。

1. 預備鈴響時即可入場，但至考試開始鈴響前，不得翻閱試題，並不得書寫、畫記、作答。
2. 考試開始鈴響時，即可開始作答；考試結束鈴響畢，應即停止作答。
3. 入場後於考試開始 40 分鐘內不得離場。
4. 全部答題均須在試卷（答案卷）作答區內完成。
5. 試卷作答限用藍色或黑色筆（含鉛筆）書寫。
6. 試題須隨試卷繳還。


國立中正大學 112 學年度碩士班招生考試試題

科目名稱：電子學


本科目共 4 頁 第 1 頁

系所組別：電機工程學系-電磁晶片組、計算機工程組、晶片系統組

 1. (10%) In the following circuit, the transistor Tr. operates with $V_T=0.5\text{ V}$, $\mu_n C_{OX} W/2L=0.2\text{ mA/V}^2$, and no channel length modulation effect should be considered. Please properly choose (a) (5%) R_D and (b) (5%) R_{G1} to let the mid-band voltage gain become -4 as $V_{DS,q}$ being 2 V



 2. (15%) For a common-source MOSFET amplifier, the transistor Tr. has $V_T = 1\text{ V}$, $\mu_n C_{OX} W/L = 0.2\text{ mA/V}^2$, $C_{gs} = 3\text{ pF}$, $C_{gd} = 2.5\text{ pF}$ and $V_A = 20\text{ V}$, and no channel length modulation effect should be considered. Both of coupling capacitors (C_1 and C_2) are large enough to be short circuits at high frequency
- (a) (5%) What is the 3dB bandwidth if $R_i = 0$
- (b) (5%) Find the 3dB bandwidth if $R_i = 10\text{ k}\Omega$.
- (c) (5%) What kind of roles are played by C_1 and C_2 ?



3. (25%) A MOS differential amplifier with $\pm 1\text{-V}$ supplies and 1 mW maximum quiescent power dissipation to provide the differential voltage gain A_d of which being 10 V/V .
- (a) (5%) What is the required V_{ov} to support the input differential signal v_{id} ($=v_{GS1} - v_{GS2}$) being 0.25 V .
- (b) (5%) What's the transconductance of Q_1 and Q_2 ?
- (c) (5%) Please explain the role of R_D and the limitation to choose its value?
- (d) (5%) Assume $k'_n = 500\text{ }\mu\text{A/V}^2$, to specify the required aspect ratio (W/L) as neglecting the Early effect.


國立中正大學 112 學年度碩士班招生考試試題

科目名稱：電子學

本科目共 4 頁 第 2 頁

系所組別：電機工程學系-電磁晶片組、計算機工程組、晶片系統組

 (e) (5%) Please summarize the effects of R_{SS} happened to differential voltage gain A_d and common-mode voltage gain A_{CM} .



國立中正大學 112 學年度碩士班招生考試試題

科目名稱：電子學

本科目共 4 頁 第 3 頁

系所組別：電機工程學系-電磁晶片組、計算機工程組、晶片系統組

4. Fig. P4 shows two applications of op amp. Assuming the op amps used in Fig. P4 are ideal, please answer the following questions:

(1) Find the I_o and R_o indicated in Fig. P4(a). (5%)

(2) If the op amp used in Fig. P4(b) has offset voltage (V_{OS}) of 4 mV, input bias current (I_B) of 1 μ A, and input offset current (I_{OS}) of 0.1 μ A, find the largest dc offset voltage at the output. (10%)

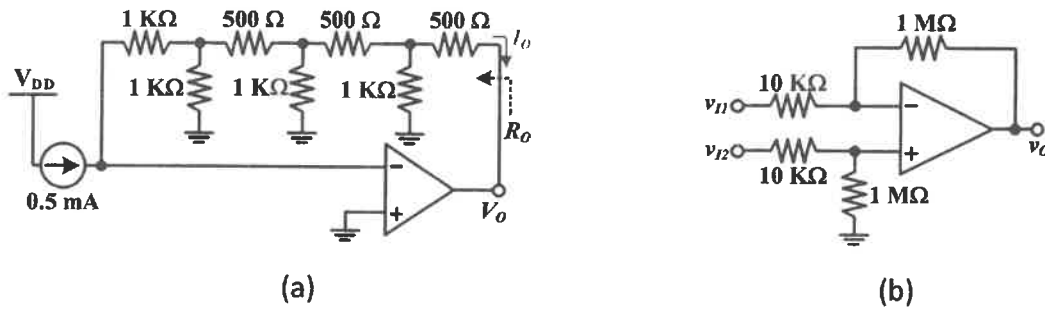


Fig. P4

5. Fig. P5 shows a feedback amplifier, where transistors M_1 , M_2 , and M_3 are biased at saturation region with a bias current of 0.2 mA and an overdrive voltage of 0.4 V. Meanwhile, each current source is implemented using single transistor so that contributes an output resistance. Assume that $|V_A| = 20$ V for all transistors, please find the close-loop gain (v_o/v_i). (20%)

 


Fig. P5

6. The CMOS logic gate shown in Fig. P6 drives a load capacitance of 10 fF, where the input waveforms are periodic with a cycle time of 1 ns. Please determine the dynamic power dissipation when the logic gate drives the load capacitance with ignoring the short circuit current. (8%)

 


Fig. P6

國立中正大學 112 學年度碩士班招生考試試題

科目名稱：電子學

本科目共 4 頁 第 4 頁

系所組別：電機工程學系-電磁晶片組、計算機工程組、晶片系統組

7. The CMOS inverter shown in Fig. P7 is fabricated using the following parameters: $V_{TH,n} = |V_{TH,p}| = 0.5 \text{ V}$, $2\mu_p C_{ox} = \mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, please find the output voltage of V_Y . (7%)

 


Fig. P7