



系組：電機系乙組、電機系海外

准考證號碼：

科目：電路學

(請考生自行填寫)

注意事項	一、請先檢查准考證號碼、報考系(組)別、考試科目名稱，確定無誤後再作答。
	二、所有答案應寫於答案紙上，否則不予計分。
	三、作答時應依試題題號，依序由上而下書寫，作答及未作答之題號均應抄寫。

1. Determine the values of the mesh currents,  $i_1$  and  $i_2$ , for the circuit shown in Figure 1. (20%)

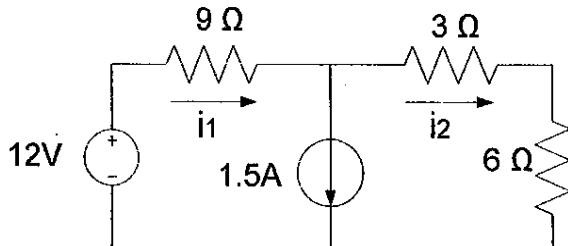


Fig. 1

2. For the circuit of Figure 2, specify the value of the resistance  $R_L$  that will cause current  $i_L$  to be -2A. (20%)

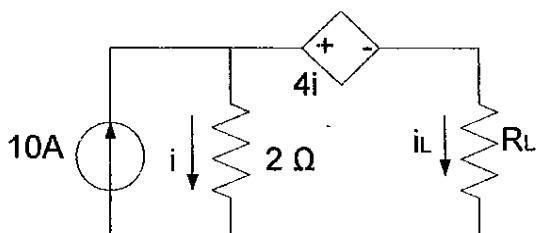


Fig. 2

3. Find  $V_0$  for the circuit shown in Figure 3. Assume an ideal operational amplifier. (20%)

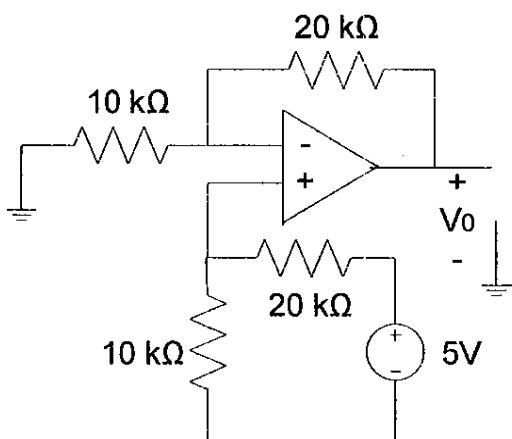


Fig. 3

4. Find the steady-state voltage  $V_0$  for the circuit of Figure 4. (20%)

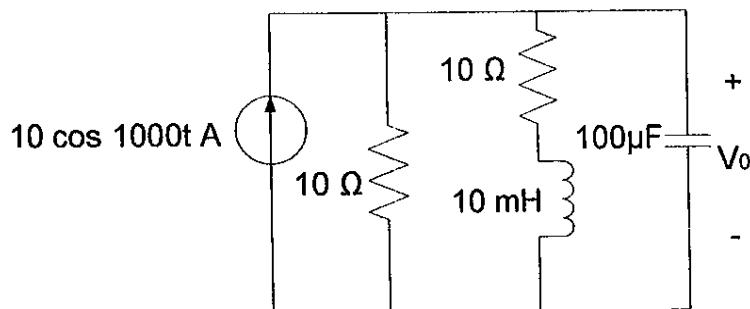


Fig. 4

5. Consider the circuit shown in Figure 5. The input to the circuit is the voltage of the voltage source, 24V. The output of this circuit, the voltage across the  $6\Omega$  resistor, is given by  $V_0(t)=12 - 6 e^{-0.35 t}$  V when  $t>0$ . Determine the values of the inductance, L, and of the resistances,  $R_1$  and  $R_2$ . (20%)

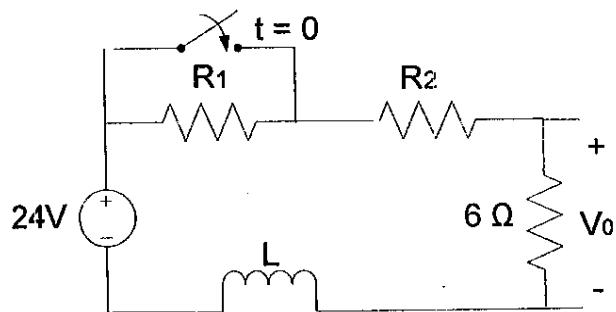


Fig. 5