

國立成功大學

113學年度碩士班招生考試試題

編 號：178、187、193

電機工程學系

系 所：電腦與通信工程研究所

電機資訊學院-微電、奈米聯招

科 目：電子學


日 期：0201

節 次：第 1 節


備 註：可使用計算機

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

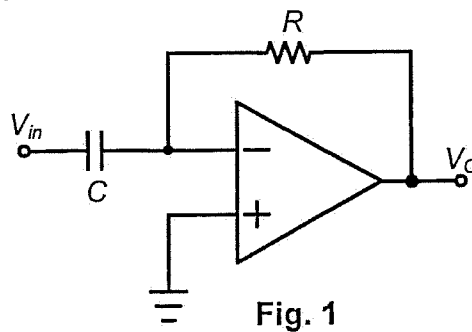1. Fig. 1 uses an ideal op amp to design a differentiation circuit for which the time constant is 10^{-3} s using a 10-nF capacitor. (16%)
 - (a) What is the value of resistor (R)? (4%)
 - (b) What are the gains and phase shifts found for this circuit at one-tenth and 10 times the unity-gain frequency? (4%)
 - (c) A series input resistor is added to limit the gain magnitude at high frequencies to 100 V/V. What is the associated 3-dB frequency? (4%)
 - (d) What gain and phase shift result at 10 times the unity-gain frequency? (4%)



2. In the common-gate amplifier circuit of Fig. 2, Q_2 and Q_3 are matched. $K'_n(W/L)_n = K'_p(W/L)_p = 4 \text{ mA/V}^2$, and all transistors have threshold voltage $|V_t| = 0.8 \text{ V}$ and Early voltage $|V_A| = 20 \text{ V}$. The signal v_{sig} is a small sinusoidal signal with no dc component. (20%)
 - (a) Neglecting the effect of V_A , find the required value of V_{BIAS} . (4%)
 - (b) Find the values of g_{m1} and r_o for all transistors. (4%)
 - (c) Find the input resistance (R_{in}). (4%)
 - (d) Find the output resistance (R_{out}). (4%)
 - (e) Calculate the voltage gains v_o/v_i and v_o/v_{sig} . (4%)

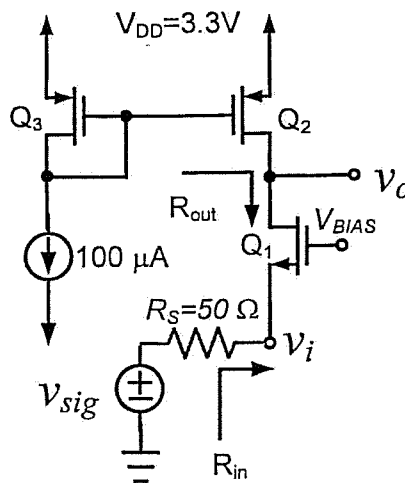

3. The feedback current amplifier in Fig. 3 utilizes two identical NMOS transistors sized so that at $I_D=0.2$ mA they operate at $V_{OV}=(V_{GS}-V_t)=0.2$ V. Both devices have threshold voltage $V_t=0.5$ V and Early voltage $V_A=10$ V. (14%)

(a) Find the voltage gain $A_f = I_o/I_s$. (4%)

(b) Find the input resistance (R_{in}) and output resistance (R_{out}). (10%)

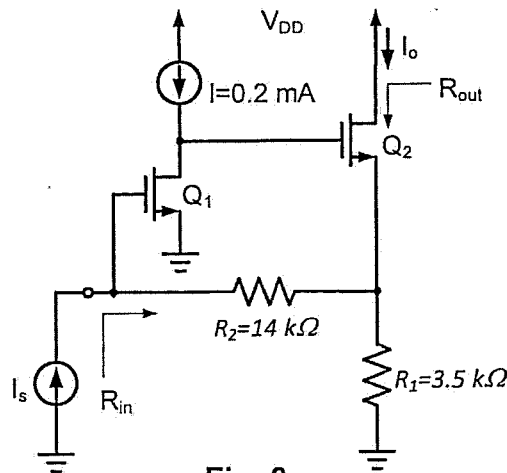


Fig. 3

4. The op amp in the circuit of Fig. 4 has an open-loop gain of 10^6 and a single-pole rolloff with $\omega_{3dB} = 100$ rad/s. Please find the close-loop transfer function, including its zero and poles. (10%)

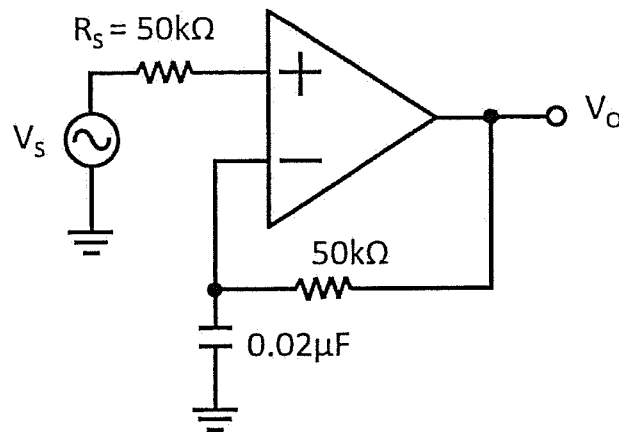


Fig. 4

5. Figs. 5(a) and (b) show two types of oscillators, and the configuration in Fig. 5(b) is the most commonly used configuration nowadays. Please answer the following questions. (20%)

(a) Describe the Barkhausen criterion. (4%)

(b) Draw the small signal model and derive the loop gain of Fig. 5(a). (6%)

(c) According to the results in (b), prove that the oscillation frequency $\omega_0 = \frac{1}{\sqrt{L \frac{C_1 C_2}{C_1 + C_2}}}$. (4%)

(d) What is the role of inverter with feedback resistor R_F in Fig. 5(b). (6%)

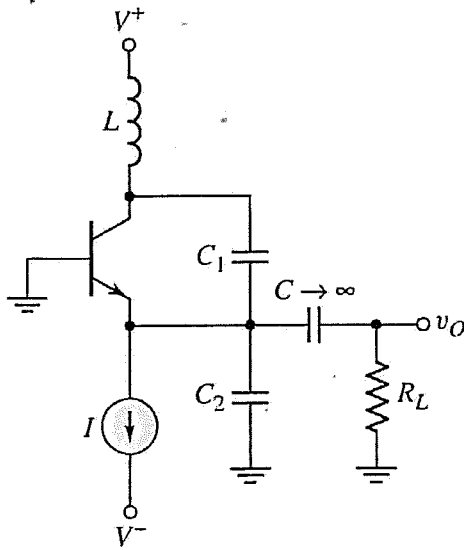


Fig. 5(a)

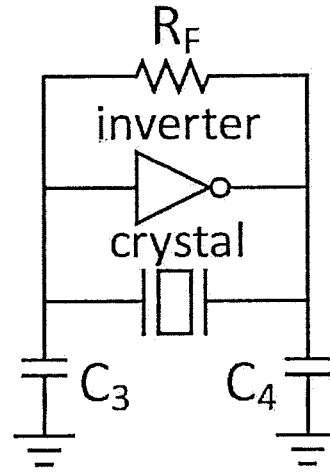


Fig. 5(b)

6. The BJTs in the circuits of Fig. 6 have $\beta_P=20$, $\beta_N=200$, $|V_{BE}|=0.6V$ and $|V_A|=100V$. (20%)

- (a) Please find the value of I_C in Fig. 6(a). (7%)
- (b) Please find the value of V_C in Fig. 6(b). (7%)
- (c) Please find the value of R_{in} in Fig. 6(b). (6%)

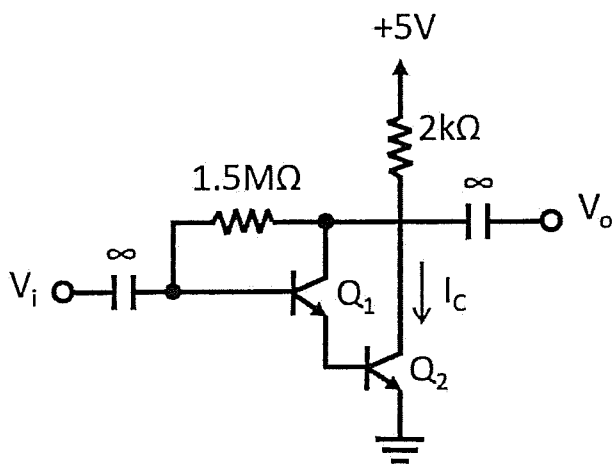


Fig. 6(a)

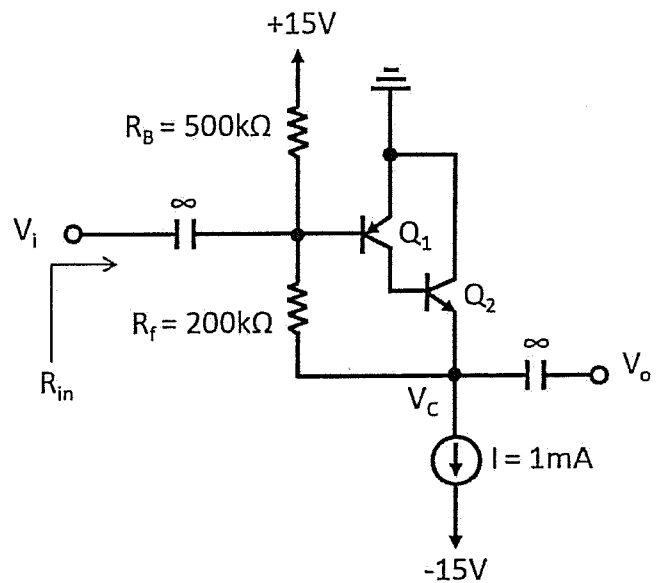


Fig. 6(b)