

國立中正大學
113 學年度碩士班招生考試
試題

[第 2 節]

科目名稱	電子學
系所組別	電磁晶片組 電機工程學系- 計算機工程組 晶片系統組

—作答注意事項—

※作答前請先核對「試題」、「試卷」與「准考證」之系所組別、科目名稱是否相符。

1. 預備鈴響時即可入場，但至考試開始鈴響前，不得翻閱試題，並不得書寫、畫記、作答。
2. 考試開始鈴響時，即可開始作答；考試結束鈴響畢，應即停止作答。
3. 入場後於考試開始 40 分鐘內不得離場。
4. 全部答題均須在試卷（答案卷）作答區內完成。
5. 試卷作答限用藍色或黑色筆（含鉛筆）書寫。
6. 試題須隨試卷繳還。

國立中正大學 113 學年度碩士班招生考試試題

科目名稱：電子學


本科目共 2 頁 第 1 頁

系所組別：電機工程學系-電磁晶片組、計算機工程組、晶片系統組

If a parameter un-given in the question, you can specify it in the answer sheet.


1. (20%) For an output current whose nominal value is $100 \mu\text{A}$, and Q_1 and Q_2 are matched with channel length of $0.5 \mu\text{m}$, channel widths of $5 \mu\text{m}$, $V_t=0.4 \text{V}$ and $k'_n=500 \mu\text{A}/\text{V}^2$. Early voltage is $5 \text{V}/\mu\text{m}$.

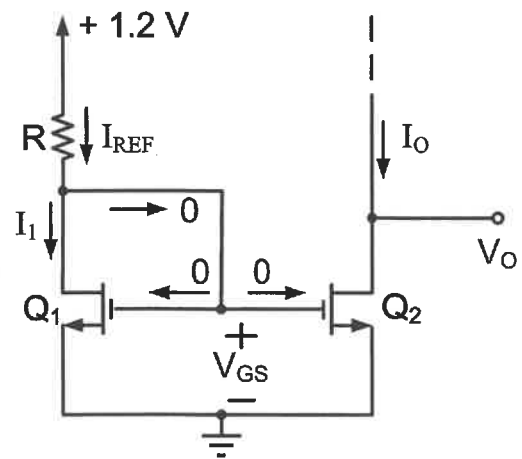- (a) (5%) What is the required value of R ?
 (b) (5%) What is the lowest possible value of V_o ?
 (c) (5%) Find the output resistance of current source.
 (d) (5%) Find the change in output current resulting from a $+0.5 \text{V}$ change in V_o .



2. (20%) Three MOSFETs are sized to operate at $|V_{ov}|=0.3\text{V}$. Let $|V_t|=0.5\text{V}$ and $|V_A|=20\text{V}$, the current sources utilize single transistors and thus have output resistances equal to r_o .

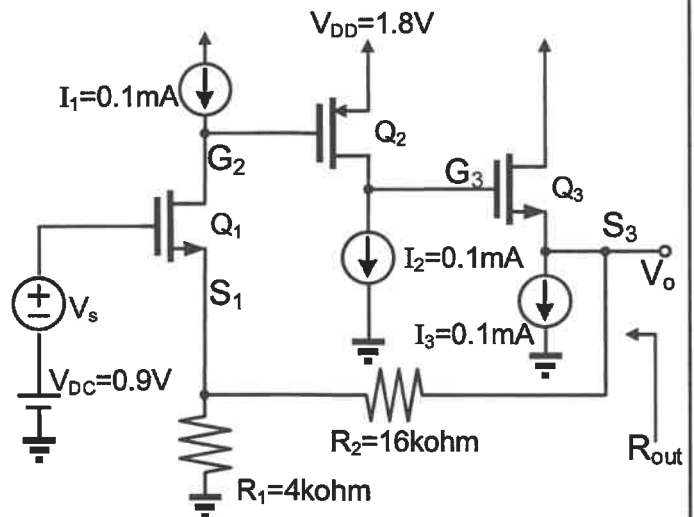- (a) (5%) If V_s has a zero dc component, find the dc voltages at nodes S_1 , G_2 , S_3 , and G_3 . Verify that each of the current sources has the minimum required dc voltage across it for proper operation.
 (b) (5%) Calculate the gain of each of these three stages and the overall voltage gain, A .
 (c) (5%) Find $A_f = V_o/V_s$.
 (d) (5%) Find the output resistance.



3. (20%) An NMOS transistor operating in the triode region with $v_{DS}=0.3\text{V}$ conducts $50\mu\text{A}$ for $v_{GS}=2\text{V}$ and $100\mu\text{A}$ for $v_{GS}=3\text{V}$, respectively.

- (a) (5%) What is the corresponding value of threshold voltage V_{th} ?
 (b) (5%) If $k_n'=\mu_n C_{ox}=20\mu\text{A}/\text{V}^2$, what is the device aspect ratio?
 (c) (5%) What current would be expected to flow with $v_{GS}=2.8\text{V}$ and $v_{DS}=0.25\text{V}$?
 (d) (5%) If it operates at $v_{DS}=2\text{V}$, at what value of v_{GS} will the drain-end of the MOSFET channel just become pinch-off.


國立中正大學 113 學年度碩士班招生考試試題

科目名稱：電子學

本科目共 2 頁 第 2 頁

系所組別：電機工程學系-電磁晶片組、計算機工程組、晶片系統組

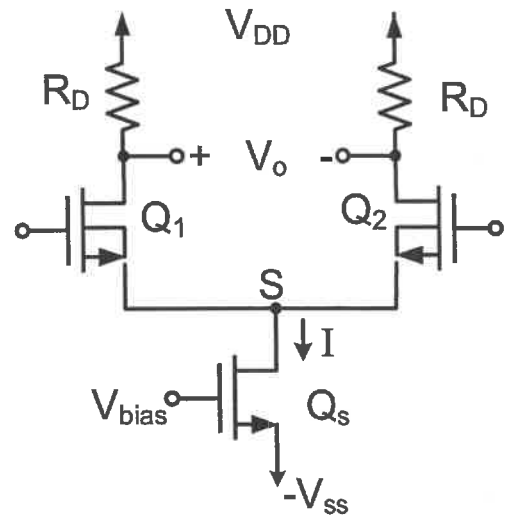4. (20%) The current source in a MOSFET differential amplifier provides constant current $I=500 \mu\text{A}$ and its equivalent resistance R_{SS} and capacitance C_{SS} are $100 \text{ k}\Omega$ and 0.1 fF , respectively. The parameters of Q_1 and Q_2 are $V_A = 25 \text{ V}$, $C_{gs} = 30 \text{ fF}$, $C_{gd} = 5 \text{ fF}$, and $C_{db} = 5 \text{ fF}$. The drain resistor R_D is $30 \text{ k}\Omega$. Transistors are biased with overdrive voltage $V_{ov} = 0.3 \text{ V}$. Also, there is a 100 fF capacitive load (C_L) existed between each drain and ground.



- (5%) Find the mid-band differential gain A_d . (5%)
- (5%) If the series resistance (R_{sig}) of input signal source for each gate terminal is $20 \text{ k}\Omega$, please estimate the upper 3-dB frequency f_H by open-circuit time-constant method.
- (5%) Find the common-mode gain response $A_{cm}(j\omega)$.
- (5%) Which is the dominate corner frequency in CMRR response.

5. (20%) A noninverting op amp provides a direct implementation of the feedback loop. Assume that the op amp has infinite input resistance and zero output resistance.

- (5%) Find an expression for the feedback factor β .
- (5%) If the open-loop voltage gain $A = 10^5$, find R_2/R_1 to obtain a closed-loop voltage gain A_f of 10
- (5%) What is the amount of feedback in decibels?
- (5%) If $V_s = 1 \text{ V}$, find V_o , V_f , and V_i .

