

※ 考生請注意：本試題可使用計算機，並限「考選部核定之國家考試電子計算器」機型

1. (a). (6%) Describe and explain the Resolution Bandwidth (RBW) and Video Bandwidth (VBW) in Superheterodyne Spectrum Analyzer.  
 (b). (6%) Calculate the tilt angle if in-phase 120-Hz ac signals are applied to the deflection plates so that  $E_v$  is 35V and  $E_h$  is 15-V peak with the same amplitude scale in the X-Y mode of the Oscilloscope.
2. (8%) The output of a DC power supply falls from 20 V to 19. 83 V when the ac input drops by 10%. The output also falls from 20 V to 19.78 V when the load current goes from zero to its maximum level. Determine the line and load regulation.
3. (a). (10%) Please draw the block diagram of a frequency counter and explain it.  
 (b). (5%) Find the period in seconds of a signal, if the DCA (Decimal Counting Assembly) count is 3535 and the time base frequency is 35 kHz.
4. Use the Hay Bridge to measure the unknown inductor  $L_x$  to find its equivalent resistance and inductance. The signal frequency is 200 Hz .The Hay bridge has  $R_1=1.5\text{ k}\Omega$ ,  $R_3=100\ \Omega$ ,  $R_4=1\text{ k}\Omega$ , and  $C_3=0.05\text{ mF}$ , shown in Fig.1.  
 (a). (5%) Is it proper to use the Hay Bridge to measure the  $L_x$ ? Why?  
 (b). (5%) Please transfer it to Maxwell's bridge and calculate  $L_s$ ,  $R_s$ .  
 (c). (5%) Determine the values of the  $R_1$  and  $R_3$  in Maxwell's bridge with given  $C_3=0.05\text{ mF}$ ,  $R_4=1\text{ K}\Omega$  and the same  $L_s$  value in (b).

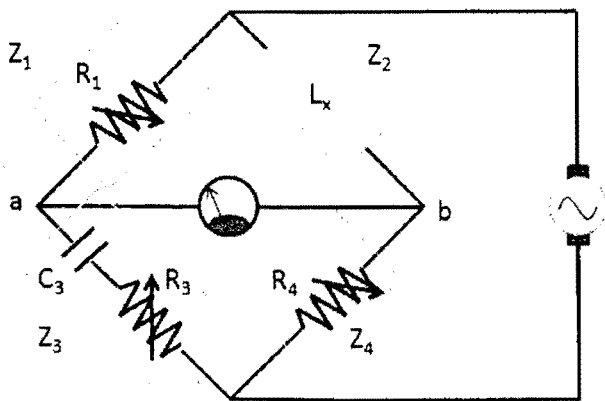


Fig.1

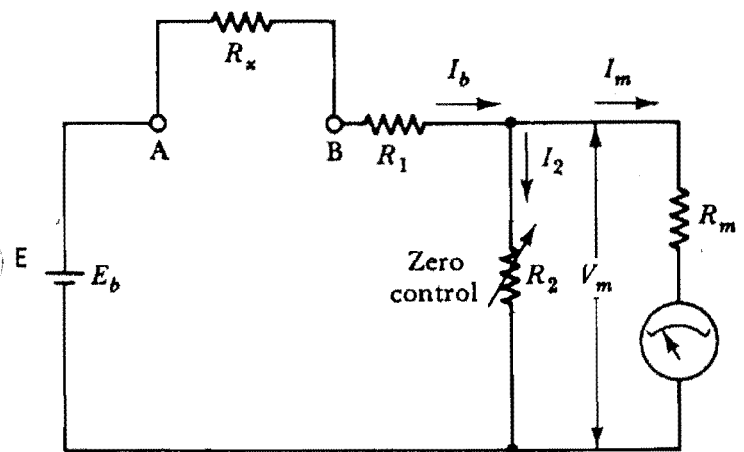


Fig. 2

5. A series ohmmeter (Fig. 2) that has a standard internal resistance of  $R_1 = 50\text{ k}\Omega$  uses a meter with  $FSD = 75\ \mu\text{A}$  and  $R_m = 100\ \Omega$ . The meter shunt resistance is  $R_2 = 300\ \Omega$ , and the battery voltage is  $E_b = 5\text{ V}$ .  
 (a) (10%) Determine the resistance measured at 0, 25%, 50%, 75%, and 100% of full-scale deflection.  
 (b) (5%) Determine the new resistance to which  $R_2$  must be adjusted when  $E_b$  falls to 4 V.

(背面仍有題目,請繼續作答)

系所組別： 電機工程學系戊組

考試科目： 電儀表學

考試日期： 0226，節次： 2

※ 考生請注意：本試題可使用計算機，並限「考選部核定之國家考試電子計算器」機型

6. (10%) Some components such as four-terminal resistor are used to reduce the loading effect in measurement instruments. Briefly explain the function of four-terminal resistor in an Ammeter. (Fig. 3)

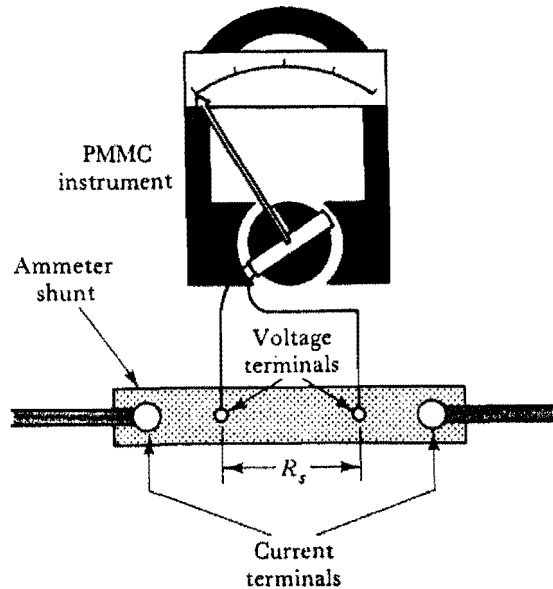


Fig. 3

7. (15%) Draw the patterns on the TDR (TIME-DOMAIN REFLECTOMETRY) for the circuits shown in Fig. 4.



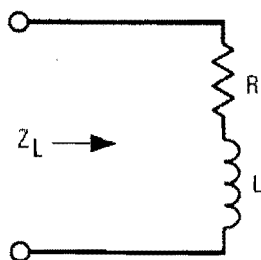


Fig. 4 (a)

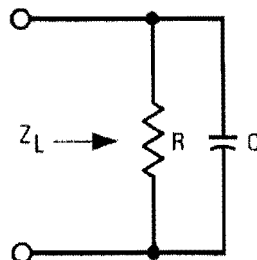

(b)

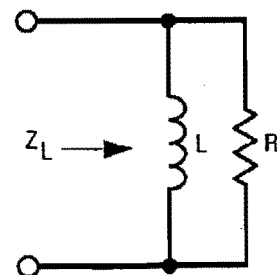

(c)

8. (10%) Describe the **compensation techniques** for the impedance analyzer (IA) measurements? (Fig. 5)

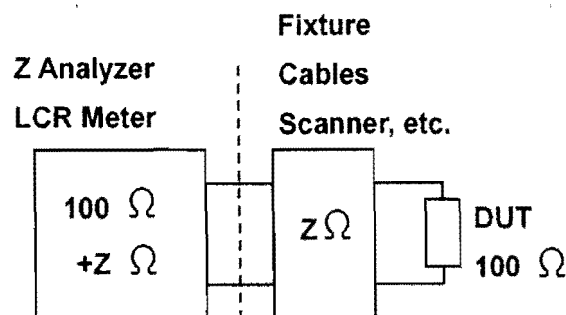


Fig. 5