

1. Consider the circuit of Fig. 1 with  $V_{BB}=1.7\text{ V}$ ,  $R_B=100\text{ k}\Omega$ ,  $V_{CC}=10\text{ V}$ , and  $R_C=5\text{ k}\Omega$ . Let the transistor  $\beta=100$ . The input signal  $v_i$  is a triangular wave of  $0.4\text{ V}$  peak-peak. (a) Find approximate values for the peak-to-peak amplitude of  $i_b$  and of  $v_{be}$ . (10%) (b) What is the voltage gain of the amplifier? (10%)
2. The amplifier of Fig. 2 consists of two identical common-emitter amplifiers connected in cascade. For  $V_{CC}=15\text{ V}$ ,  $R_1=100\text{ k}\Omega$ ,  $R_2=47\text{ k}\Omega$ ,  $R_E=3.9\text{ k}\Omega$ ,  $R_C=6.8\text{ k}\Omega$ ,  $R_{sig}=5\text{ k}\Omega$ , and  $R_L=2\text{ k}\Omega$ , find the overall voltage gain  $v_o/v_{sig}$ . (20%)
3. (a) Please use the power supply, capacitance and resistance to design a band pass filter circuit (10%).

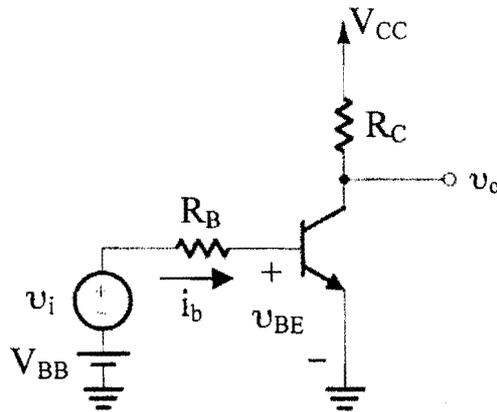


Fig. 1

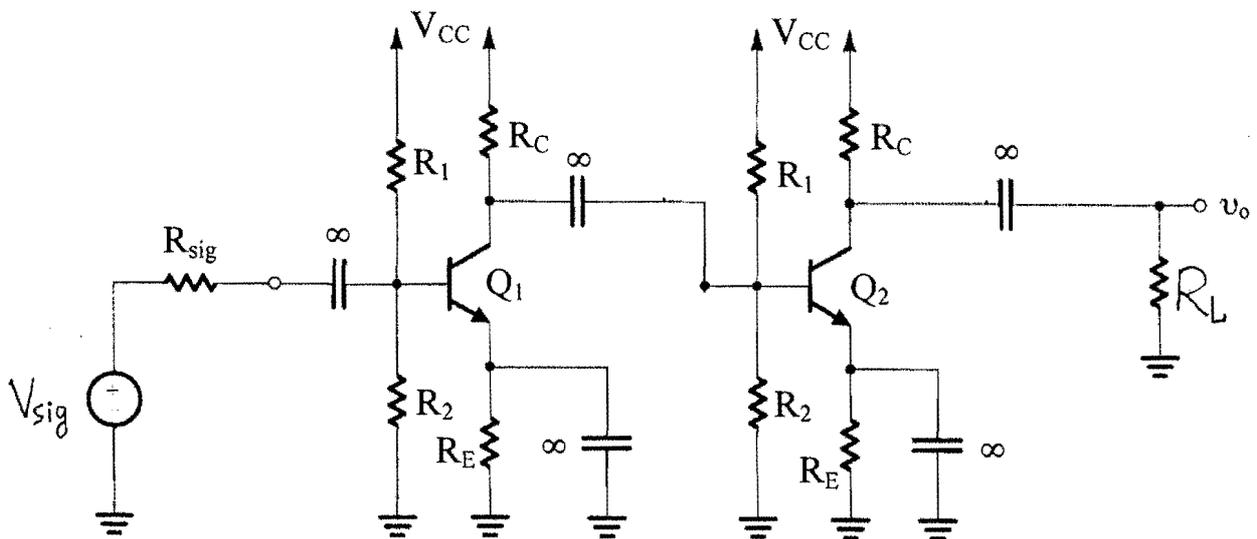


Fig. 2

(背面仍有題目,請繼續作答)

4. Figure 3 shows a MOSFETs differential circuit.  $Q_1$  and  $Q_2$  are matched.  $Q_3$  in the circuit operated in the triode region. Please find

- (a) With  $v_{G1}=v_{G2}=0$ , and assuming  $Q_1$  and  $Q_2$  are in saturation, what dc voltages appear at the sources of  $Q_1$  and  $Q_2$ . Please express the dc voltages in terms of the overdrive voltage  $V_{OV}$  at which each of  $Q_1$  and  $Q_2$  operates, and  $V_t$ .
- (b) For the situation in (a), what current flows in  $Q_3$ ? What overdrive voltage  $V_{OV3}$  is  $Q_3$  operating at, in terms of  $V_C$ ,  $V_{OV}$ , and  $V_t$ ?
- (c) For  $v_{G1}=v_{id}/2$ , and  $v_{G2}=-v_{id}/2$  where  $v_{id}$  is a small signal please describe the status of the  $Q_3$ . Now if all transistors have the same  $W/L$ , express  $r_{DS}$  of  $Q_3$  in terms of  $V_{OV}$ ,  $V_{OV3}$ , and  $g_{m1,2}$ .

(25%)

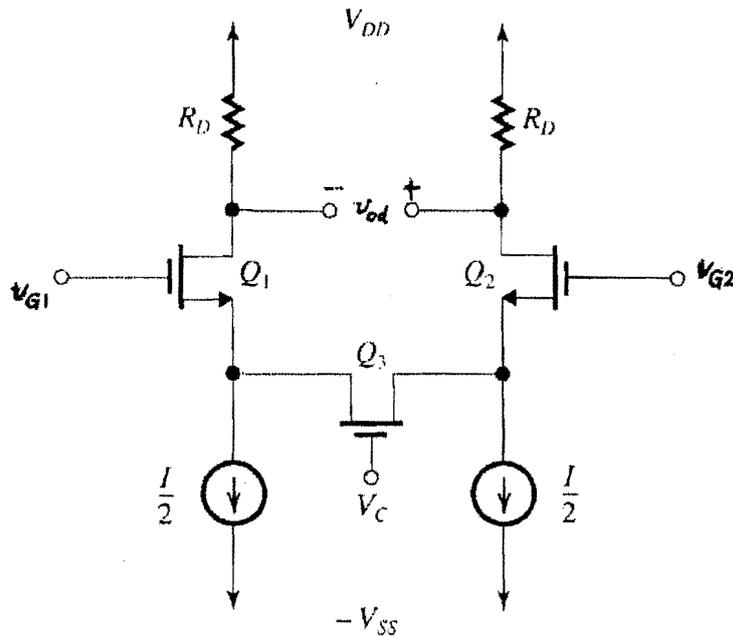


Fig. 3

5. Figure 4 shows an amplifier formed by cascading two CS stages. Each of  $Q_1$  and  $Q_2$  is operated at an overdrive voltage of  $0.2V$  and  $|V_A|=10V$ . The transistor capacitances are as follows:  $C_{gs}=20fF$ ,  $C_{gd}=5fF$ , and  $C_{db}=5fF$

- (a) Find the dc voltage gain.
- (b) Find the input capacitance at the gate of  $Q_1$ , using the Miller approximation.

- (c) Use the capacitance in (b) to determine the frequency of the pole formed at the amplifier input. Let  $R_{sig}=10k\Omega$ .
- (d) Use the Miller approximation to find the input capacitance of  $Q_2$  and hence determine the total capacitance at the drain of  $Q_1$ .
- (e) Use the capacitance found in (d) to get the frequency of the pole formed at the interface between the two stages.
- (f) Determine the total capacitance at the output node and find the frequency of the pole formed at the output node.
- (g) Does the amplifier have a dominant pole? If so, at what frequency? (25%)

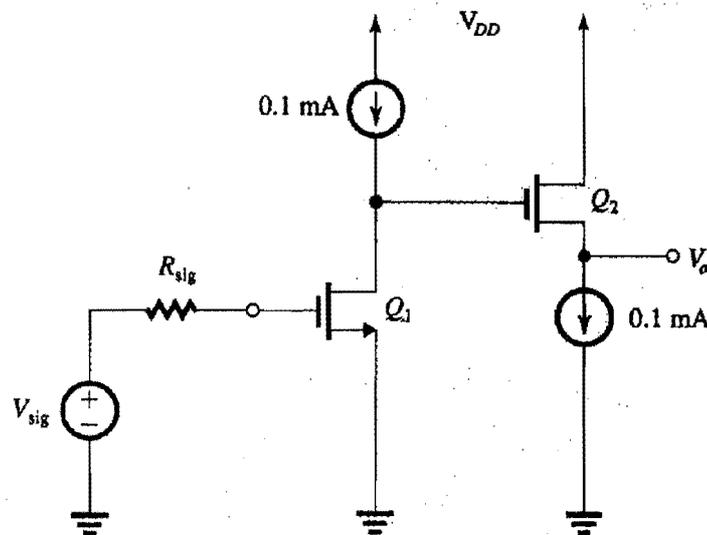


Fig. 4