

※ 注意：請於試卷上「非選擇題作答區」內依序作答，並應註明作答之大題及其題號

第一部分為選擇題，答案可能不只一個，需全對才給分。共 10 題，每題 5 分。

1. Please select the correct one(s) about the characteristics of the ideal Op amp.
 - (A) Infinite input impedance
 - (B) Infinite output impedance
 - (C) Infinite common-mode gain
 - (D) Infinite closed-loop gain
 - (E) Infinite bandwidth
2. Please select the correct one(s) about the characteristics of a real silicon diode.
 - (A) As temperature increases, the voltage required to maintain a constant current will also increase.
 - (B) As temperature increases, the saturation current will also increase.
 - (C) A diode in reverse-biased can be used for voltage regulation.
 - (D) A diode in reverse biased will not conduct any current.
 - (E) The larger the size, the higher the saturation current.
3. Please select the correct one(s) about the characteristics of an *npn* silicon BJT.
 - (A) The current is mainly composed of electron drift current under base-emitter junction forward bias.
 - (B) The current gain β in active mode operation is smaller than the β in saturation mode operation.
 - (C) The common-base configuration has better high-frequency response than the common-emitter one.
 - (D) If we consider Early effect, the small-signal gain will decrease.
 - (E) Breakdown voltage BV_{CBO} is usually half BV_{CEO}
4. Please select the correct one(s) about the characteristics of a silicon NMOS.
 - (A) The current is mainly composed of electron drift current under drain-source terminal forward bias.
 - (B) Increasing oxide thickness will cause the transconductance g_m to decrease.
 - (C) The Body effect will reduce threshold voltage and increase drain current.
 - (D) Including a resistor in the source lead of the common source stage can effectively increase gain.
 - (E) In general, an NMOS provides more gain compared to an *npn* BJT when applying in the amplifier design.
5. Please select the correct one(s) about the characteristics of different types of amplifiers.
 - (A) We stack a common-emitter transistor on top of a common-base transistor to raise the output resistance.
 - (B) A MOS cascode amplifier with a cascode current-source load achieves a gain of $(g_m r_o)^2$.
 - (C) The Widlar current source provides a way to implement a low-valued constant-current source that also has a high output resistance.
 - (D) In the MOS differential pair amplifier, to steer the current completely to one side of the pair, a difference input voltage of $2V_{OV}$ is needed.
 - (E) Differential amplifiers do not need bypass and coupling capacitors.
6. Consider a 10-output current mirror in Fig. 1. Assume that all transistor are matched and have finite $\beta = 100$ and ignoring the effect of finite output resistances. If $I_{REF} = 10$ mA. What is the value of I_{10} ?
 - (A) 7 mA
 - (B) 8 mA
 - (C) 9 mA
 - (D) 10 mA
 - (E) 11 mA

見背面

7. Consider a CC-CE amplifier in Fig. 2. Assume $I_1 = I_2 = 1$ mA, Q_1 and Q_2 are matched. $\beta = 100$, $C_\pi = 13.9$ pF. $C_\mu = 2$ pF. Let the amplifier be fed with a source V_{sig} with $R_{sig} = 4$ K Ω , and load resistance $R_L = 4$ K Ω . Which RC delay term(s) may have more significant impacts on the determination of 3-dB frequency f_H ?
 (A) $C_{\mu 1} R_{\mu 1}$ (B) $C_{\mu 2} R_{\mu 2}$ (C) $C_{\pi 1} R_{\pi 1}$ (D) $C_{\pi 2} R_{\pi 2}$ (E) $C_{\pi 1} R_{\mu 2}$
8. Please select the correct one(s) about the characteristics of a CMOS logic inverter.
 (A) The basic building block of digital circuits.
 (B) The static power dissipation is the result of current flow in either 0 or 1 state or both.
 (C) The maximum frequency at which an inverter can be switched is related to its propagation delay by $f_{max} = 1/\sqrt{2}t_p$.
 (D) Larger W/L ratios can result in a reduction in t_p .
 (E) Pull-down network (PDN) comprises PMOS transistors.
9. Please select the correct one(s) about the properties of feedback amplifiers.
 (A) To build an oscillator, we need to have a positive feedback network with $A\beta \geq 1$.
 (B) The shunt-series feedback topology is best suited for voltage amplifiers.
 (C) For the feedback amplifier to be stable, most of its poles must be in the left half of the s plane.
 (D) A smaller pole Q factor will have a more flat and larger gain response.
 (E) At frequency ω_{180} , unstable amplifiers have the magnitude of the loop gain greater than one.
10. Consider the CMOS realization of a logic gate in Fig. 3. What is the output Y ?
 (A) $\overline{A + B(C + D)}$ (B) $\overline{A + BCD}$ (C) $A(B + CD)$ (D) $\overline{A + B + CD}$ (E) $A + \overline{(B + CD)}$

 


Fig. 1

 


Fig. 2

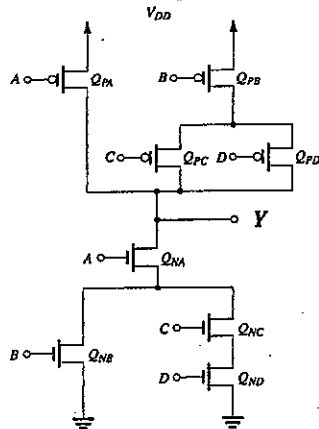


Fig. 3

第二部分為簡答題，視答對程度部分給分。

11. Draw the time-dependent output waveforms of v_o, v_+, v_- in Fig. 4. Label correctly the corresponding periods, magnitudes, time constants in your plot using $T_1, T_2, L_+, L_-, R_1, R_2, R_3, C$. (10%)
12. For the circuit in Fig. 5. Assume all the transistors, including those that implement the current sources, are operating at equal overdrive voltages of 0.3 V magnitude and have $|V_t| = 0.7$ V. In order to operate properly, each of the current sources requires a minimum voltage of $|V_{OV}|$ across its terminals. What is the range over which **both** NMOS and PMOS input stages operate? (10%)
13. The circuit in Fig. 6 is considered an amplifier. Assume that $K_n=k_p= 400 \mu A/V^2$, $V_{tn}=|V_{tp}|=1V$, $R_s= 2.5$ k Ω , $R_L=20$ k Ω and $R_G=100$ M Ω .
 - (a) What is the dc current of the NMOS transistor? (5%)
 - (b) If $v_i(t) = 0.05\sin(300t)V$, find the output voltage $v_o(t)$. (10%)
14. Consider the CMOS op amp circuit in Fig. 7. $\mu_n C_{ox} = 3\mu_p C_{ox} = 90 \mu A/V^2$, $|V_t|=0.7$ V, and $V_{DD}=V_{SS}=2.5$ V. For a particular design $I = 100 \mu A$, $(W/L)_1 = (W/L)_2 = (W/L)_5 = 200$, and $(W/L)_3 = (W/L)_4 = 100$
 - (a) What is the transistor sizing constraint to eliminate dc offset? (5%)
 - (b) Find the (W/L) ratios of Q_6 and Q_7 so that $I_G = 100\mu A$ (5%)
 - (c) Find g_m for Q_1 and Q_6 (5%)

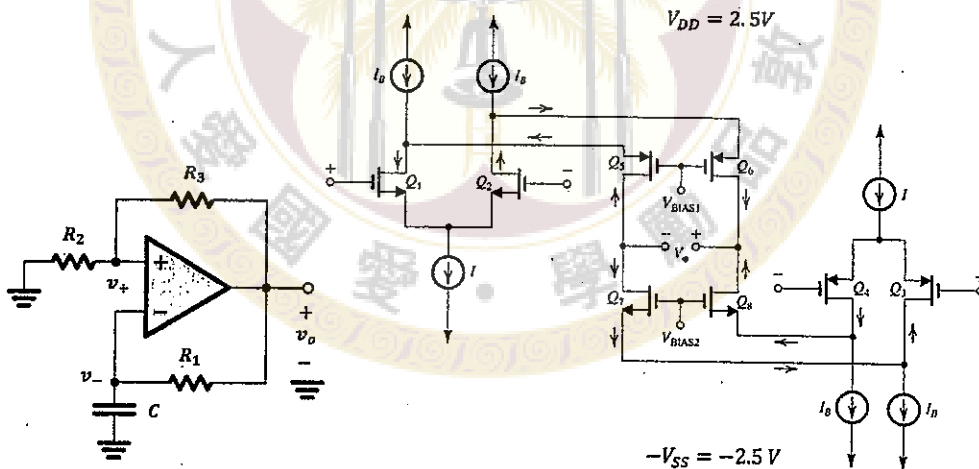


Fig. 4

Fig. 5

 


Fig. 6

 


Fig. 7