

※ 考生請注意：本試題不可使用計算機

1. (15%) For an abrupt p-n junction diode with acceptor and donor concentration of 10^{16} cm^{-3} and 10^{15} cm^{-3} , respectively. The junction area is $400 \mu\text{m}^2$. The intrinsic carrier concentration is 10^{10} cm^{-3} . ϵ_s of semiconductor is $11.7\epsilon_0$, respectively. When the diode is biased at -5V , please calculate:
 - (a) the junction build-in voltage (3%)
 - (b) the depletion width (3%)
 - (c) the depletion width on each p and n side (3%)
 - (d) the stored charges on either side of junction (3%)
 - (e) the junction capacitance C_j . (3%)

2. (15%) Please find the V_o of the circuit shown in Figure 1.

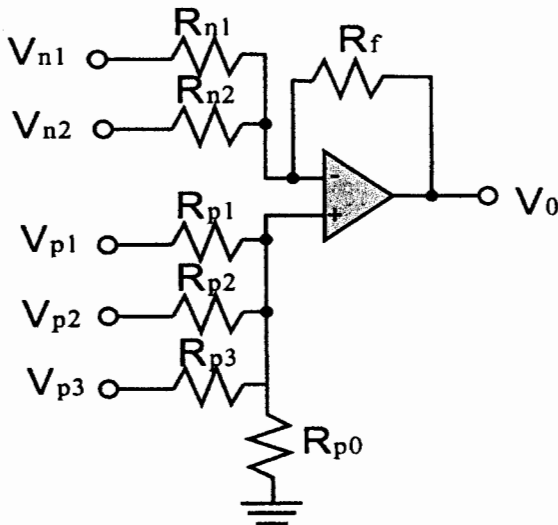


Figure 1

3. (20%) For a circuit shown in Figure 2. All transistors have $|V_t|=1\text{V}$, $\lambda=0$, $\gamma=0$, $\mu_n C_{ox}=50 \mu\text{A}/\text{V}^2$, $L=1 \mu\text{m}$, and $W=10\mu\text{m}$.
 - (a) Please find the V_2 and I_2 . (10%)
 - (b) Please also find the V_2 and I_2 when the W of the Q_3 and Q_4 is $100\mu\text{m}$. (10%)

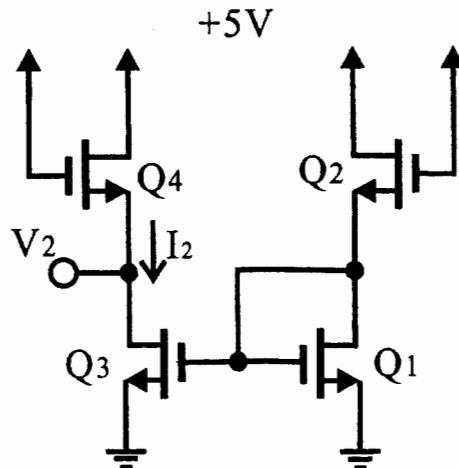


Figure 2

(背面仍有題目,請繼續作答)

※ 考生請注意：本試題不可使用計算機

4. (20%) **Figure 3** shows a folded-cascode CMOS amplifier utilizing a simple current source Q_2 , supplying a current $2I$, and a cascaded current-source (Q_4, Q_5) supplying a current I . Assume, for simplicity, that all transistors have equal parameters transconductance g_m and output resistance r_o .
- Give approximate expressions for all the resistances indicated.
 - Find the amplifier output resistance R_o .
 - Show that the short-circuit transconductance G_m is approximately equal to g_{m1} .
 - Find the overall voltage gain v_o/v_i and evaluate its value for the case $g_{m1} = 2\text{mA/V}$ and $A_0=20$.

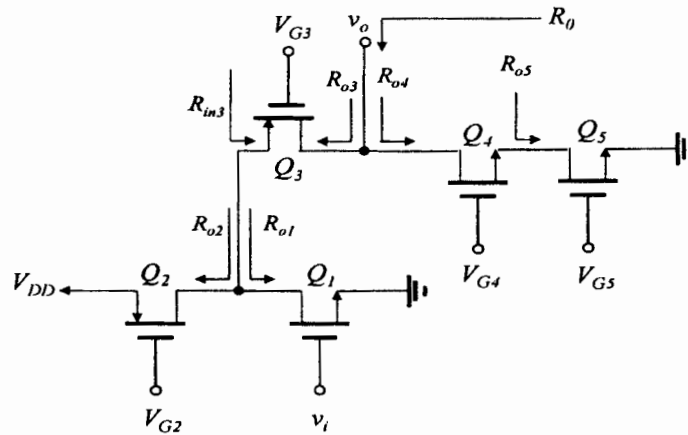


Figure 3

5. (15%) An NMOS differential amplifier employing equal drain resistors, $R_D = 47\text{ k}\Omega$ has a differential gain A_d of 20 V/V .
- What is the value of g_m for each of the two transistors?
 - If each of the two transistors is operating at an overdrive voltage $V_{OV} = 0.2\text{V}$, what must the value of I be?
 - For $v_{id} = 0$. What is the dc voltage across each R_D ?
 - If v_{id} is 20-mV peak-to-peak sine wave applied in a balanced manner but superimposed on the common-mode voltage $V_{CM} = 0.5\text{ V}$, what is the lowest value that V_{DD} must have to ensure saturation-mode operation for Q_1 and Q_2 at all times? Assume $V_t = 0.5\text{ V}$.
6. (15%) Design the inverter circuit in **Figure 4** to provide output high level $V_{OH} = 2\text{ V}$, output low level $V_{OL} = 0.1\text{ V}$, and so that the current drawn from the supply in the low-output state is $20\text{ }\mu\text{A}$. The transistor has $V_t = 0.5\text{ V}$, $\mu_n C_{ox} = 100\text{ }\mu\text{A/V}^2$, and device parameter $\lambda = 0$. Specify the required values of V_{DD} , R_D , and W/L . How much power is drawn from the supply when the output is high? When the output is low?

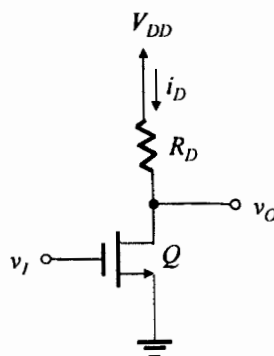


Figure 4