
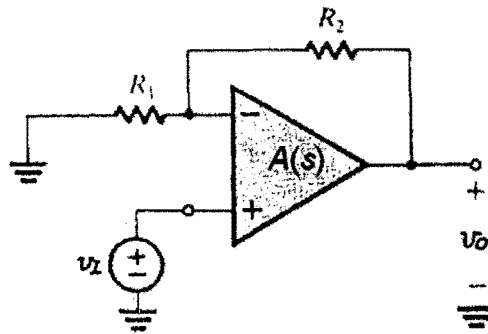


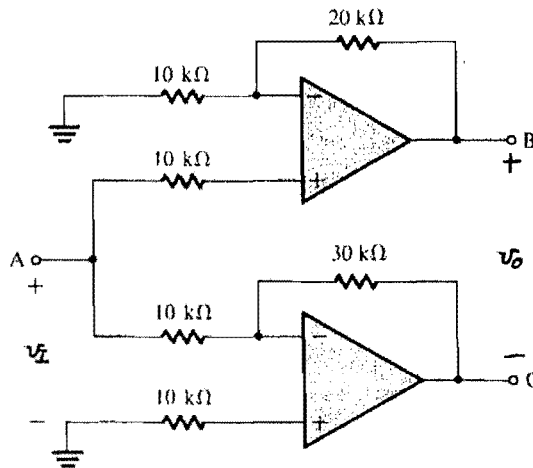1. A commercial $\mu A741$ is employed in the noninverting configuration, $R_1 = 1\text{ k}\Omega$ and $R_2 = 9\text{ k}\Omega$. The op amp has its open-loop gain (or transfer function) as $A(s) = \frac{10^4}{1 + \frac{s}{2\pi \times 100}}$. (a) Find the closed-loop gain, $G(s) \equiv v_o/v_i$. (8 分) (b) Plot the magnitude and phase responses of $G(s)$. (8 分) (c) If the input signal is $0.1\sin(2\pi \times 100 \times 10^3 t)$, that is, frequency=100 kHz and amplitude=0.1 V, obtain the output signal. (Note that $1/\sqrt{2} = 0.707$) (4 分)




2. The circuit is intended to supply a voltage to floating loads while making greatest possible use of the available power supply. (a) What is the voltage gain v_o / v_i ? (6 分) (b) Assuming that the op amps operate from $\pm 15\text{-V}$ power supplies and that their output saturates at $\pm 14\text{-V}$, what is the largest sine wave output that can be accommodated? Specify both its peak-to-peak and rms values. (Note that $1/\sqrt{2} = 0.707$) (6 分)




(背面仍有題目,請繼續作答)

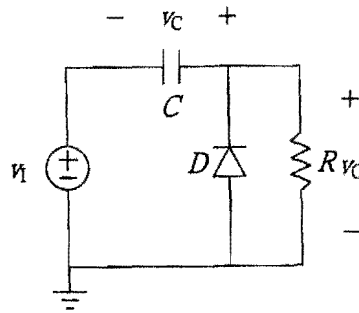3. As shown in the figure, a load resistance R is connected across the diode (D1N4148) in a clamping circuit, where $C=1\text{nF}$ and $R=100\text{K}\Omega$.




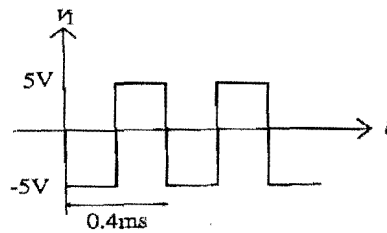The input is a square wave between -5V and $+5\text{V}$, as shown below.




If D1N4148 is modeled by the constant-voltage drop of 0.7V , plot the output waveform. (10 分)

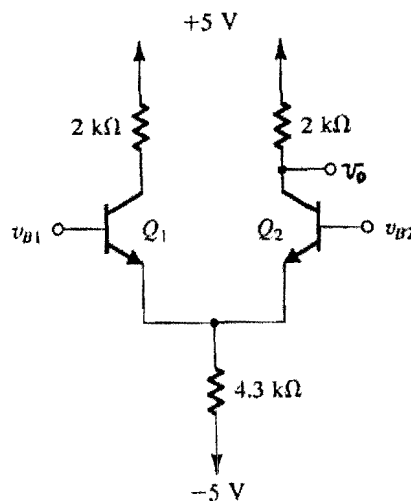4. For the following circuit, assume that $V_{BE} = 0.7\text{V}$. (a) For $v_{B1} = -v_{id}/2$ and $v_{B2} = v_{id}/2$, find the differential gain. (8 分) (b) For $v_{B1} = v_{B2} = v_{icm}$, find the common-mode gain. (8 分) (c) If $v_{B1} = 0.1\sin 2\pi \times 60t - 0.005\sin 2\pi \times 1000t$ volt and $v_{B2} = 0.1\sin 2\pi \times 60t + 0.005\sin 2\pi \times 1000t$ volt, find v_o . (4 分)



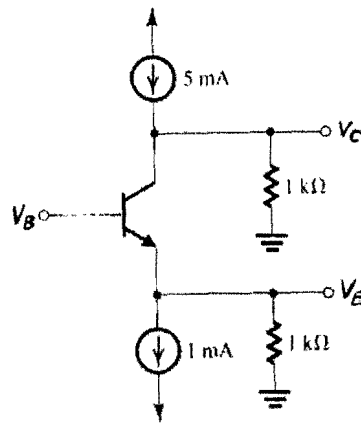5. For the circuit below, assume $\alpha \cong 1$, $V_{BE} = 0.4$ V and 0.7 V at the edge of conduction and fully conduction, respectively. (a) What are the values of V_E and V_C for $V_B = 0$ V? (6 分) (b) What's the maximum value of V_B for the cutoff of transistor? $V_C = ?$ $V_E = ?$ (6 分) (c) For what value of V_B does the transistor saturate? $V_C = ?$ $V_E = ?$ (Note that in saturation, $V_{CEsat} = 0.2$ V) (6 分)



6. A bipolar op-amp circuit with capacitor $C_C = 10$ pF placed in the negative feedback path of Q_5 . All transistors have $\beta = 100$, $|V_{BE}| = 0.7$ V, and $r_o = \infty$. (a) The DC voltages of inputs and output are assumed to be 0 V. Find the emitter currents of all transistors. (4 分) (b) Find the gain of the amplifier with $R_L = 10$ kΩ. (10 分) (c) Based on the Miller's theorem, by using the gain of Q_5 , C_C can be separated into two capacitors. After doing so, use open-circuit time constant to obtain ω_H . (6 分)

