

1. Find $i_o(t)$, $t > 0$ for the circuit in Fig. 1. [15%]

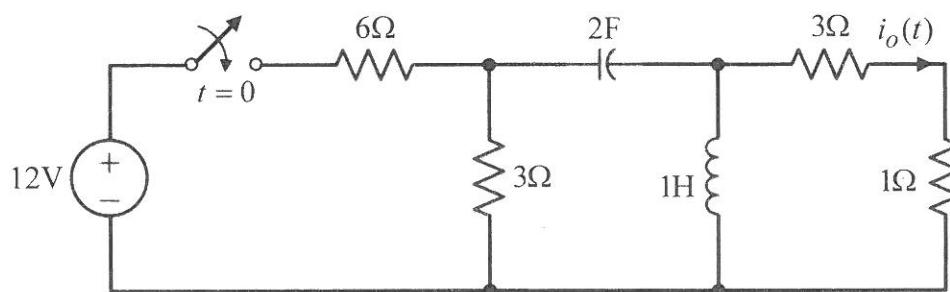


Fig. 1

2. Given the circuit in Fig. 2, design a second-order bandpass filter with a center frequency gain of -5, $\omega_0 = 10$ krad/s, and a BW = 2 krad/s. Let $C_1 = C_2 = C$ and $R_1 = 1\text{k}\Omega$, find (a) C ; (b) R_2 ; (c) R_3 ; and (d) Q of this filter. Assume that the op-amp is ideal. [20%]

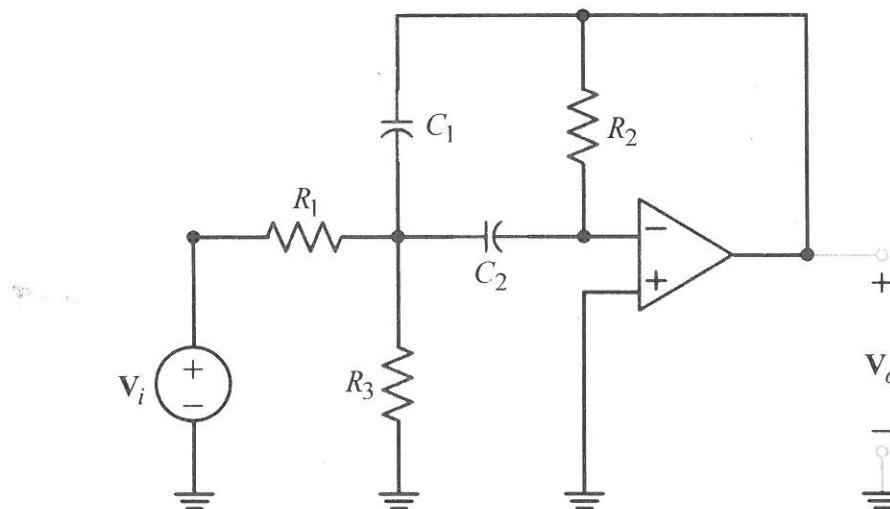


Fig. 2

3. Find the value of C in the network in Fig. 3 such that the total load has a power factor of 0.95 lagging. [10%]

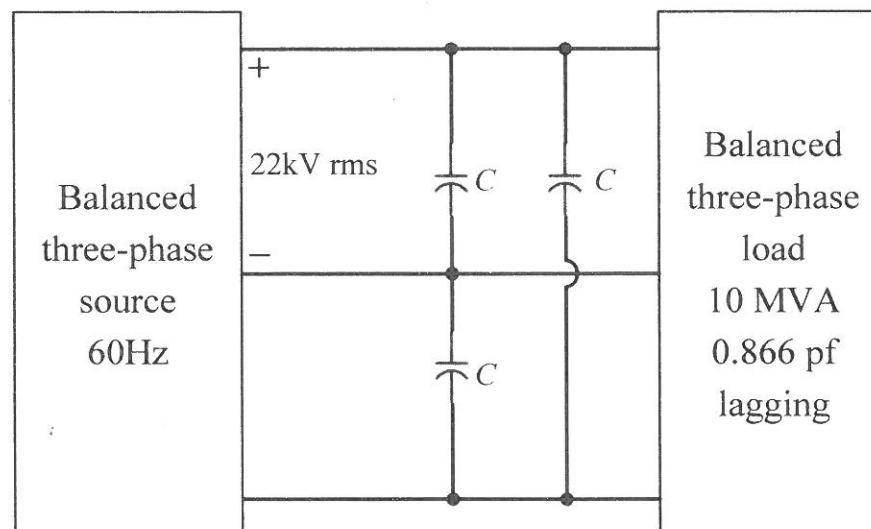


Fig. 3

4. Find $v_o(t)$ and $i_o(t)$ in Fig. 4. [10%]

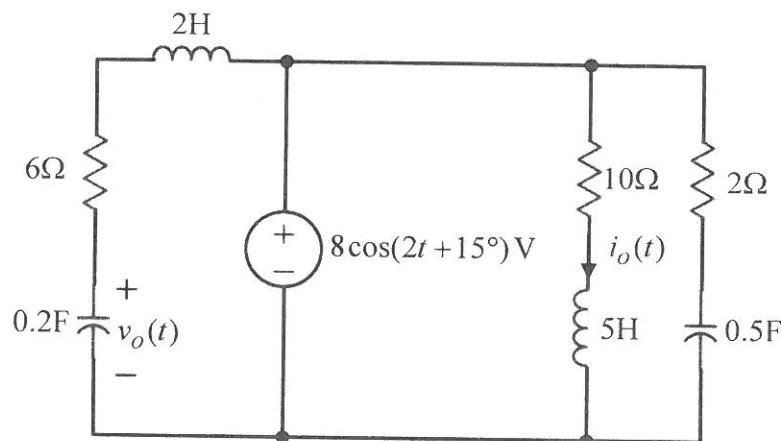


Fig. 4

5. Use Thévenin's theorem to find V_o in Fig. 5. [15%]

6. Find V_o and the loop currents I_1, I_2, I_3 in Fig. 6 using loop analysis. [20%]

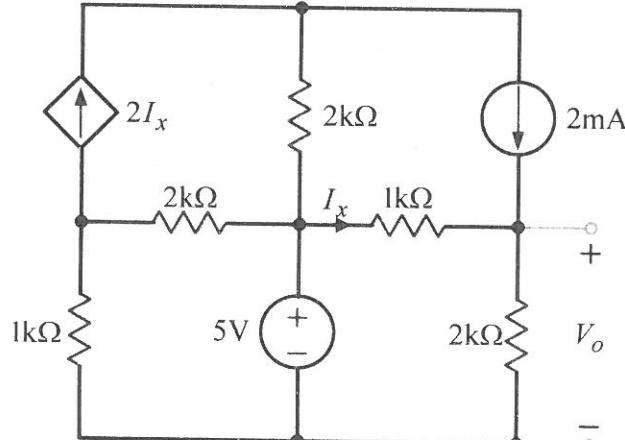


Fig. 5

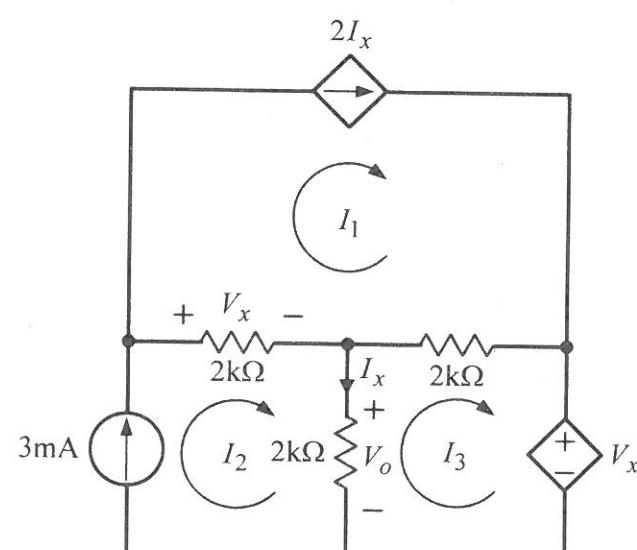


Fig. 6

7. In a balanced three-phase wye-wye system, the source is an abc -sequence set of voltages. The line impedance is $Z_{line} = 6 + j10\Omega$ and the load impedance is $Z_{load} = 12 + j6\Omega$. The load voltage on the phase-a is $\mathbf{V}_{AN} = 200\angle 20^\circ \text{ Vrms}$. Find the line voltage \mathbf{V}_{ab} of the source. [10%]