

元智大學 102 學年度研究所 碩士班 招生試題卷

系(所)別： 通訊工程學系碩士班 組別： 微波組 科目： 電子學 用紙第 / 頁共 > 頁

⊗不可使用電子計算機

1. Assume a constant-voltage mode ($D_{on} = 0.7 V$) for the diodes. (a) Plot the output voltage waveform of a full-wave rectifier as shown in Fig.1 with a sine wave input signal. 7% (b) Explain how this circuit works. 7% 14%

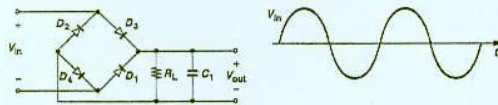


Fig.1

2. Design a self-biased common-emitter amplifier as shown in Fig.2 for voltage gain $A_v = 36.5$. Assume $V_{CC} = 1.8 V$, $I_C = 2 mA$, $I_S = 5 \times 10^{-16} A$, $\beta = 100$, $V_A = \infty$. C_1 and C_2 are blocking capacitors. (a) Determine the required value of R_C and R_B . 6% (b) Calculate V_{CE} , V_{BE} and I_B . 6% (c) Plot the small signal equivalent circuit that neglects R_B . 6% (Hint: $V_{BE} = V_T \ln(I_C / I_S)$, $\ln(10) = 2.303$, $\ln(2) = 0.693$ and $V_T = 26 mV$) 18%

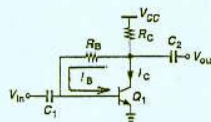


Fig.2

3. Consider the circuit as shown in Fig.3, where a source follower (M_1 and I_1) precedes a common-gate stage (M_2 and R_D). If the transconductance $g_{m1} = g_{m2}$ and $\lambda=0$ (λ is the channel-length modulation coefficient) (a) Find the overall voltage gain. 6% (b) Determine the input and output impedance. 6% (c) Plot the small signal equivalent circuit. 6% 18%

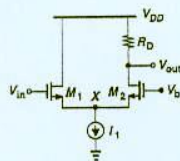


Fig.3

P149

102149

元智大學 102 學年度研究所 碩士班 招生試題卷

系(所)別： 通訊工程學系碩士班 組別： 微波組 科目： 電子學 用紙第 2 頁共 2 頁

●不可使用電子計算機

4. The CMOS operational amplifier shown in Fig. 4 has the following device geometries (in μm). (20%)

Transistor	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7	Q_8
W/L	20/0.5	20/0.5	5/0.5	5/0.5	40/0.5	10/0.5	40/0.5	40/0.5

Assume $I_{REF} = 100\mu\text{A}$, $V_{in} = 0.5\text{V}$, $V_{ip} = -0.5\text{V}$, $\mu_n C_{ox} = 100\mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 50\mu\text{A}/\text{V}^2$, $V_{DD} = V_{SS} = 2.5\text{V}$, $|V_A| = 10\text{V}$ for all devices. Find I_D , $|V_{OV}|$, g_m and r_o for all devices (12%). Also find the open-loop voltage gain in linear scale (8%).

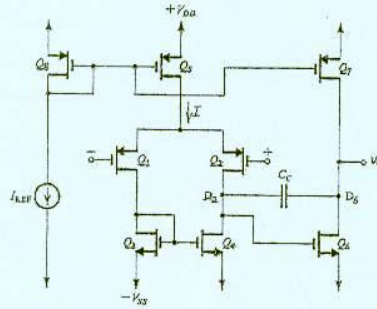


Fig. 4

5. If an amplifier has the transfer function as $T(s) = \frac{10s}{(1+s/10^2)(1+s/10^3)}$, please plot its magnitude Bode plot. (10%)
6. A series-shunt feedback amplifier is shown in Fig. 5. Find: (20%)
- The basic amplifier gain A and the feedback factor β . (10%)
 - The feedback gain A_f and the voltage gain V_o/V_s . (5%)
 - The input resistance R_{in} and output resistance R_{out} . (5%)

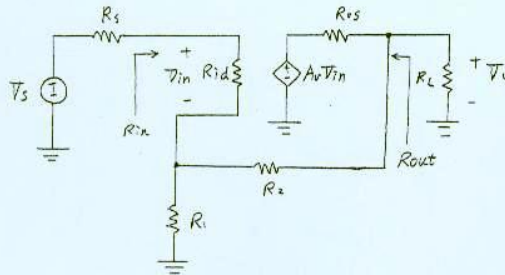


Fig. 5
P150

102150