

元智大學 102 學年度研究所 碩士班 招生試題卷

系(所)別： 電機工程學系碩士班 組別： 電子工程組 科目： 電子學 用紙第 1 頁共 2 頁

⊙不可使用電子計算機

1. (20%) Given an n -channel MOSFET with $k'_n = 100 \mu\text{A}/\text{V}^2$, $V_{tn} = 0.7 \text{ V}$, and $W/L = 10$, find the drain current i_D in the following cases:
 - (a) $v_{GS} = 3 \text{ V}$ and $v_{DS} = 1 \text{ V}$ (10%)
 - (b) $v_{GS} = 2 \text{ V}$ and $v_{DS} = 1.3 \text{ V}$ (10%)

2. (10%) Please sketch the pull-down network (PDN) of a MOS logic circuit that realizes the function $Y = \overline{A} + \overline{B}(\overline{C} + \overline{D})$.

3. (10%) Please describe the static power dissipation and dynamic power dissipation for a complementary metal-oxide-semiconductor (CMOS) logic-circuit family.

4. (55%) A two stage amplifier with feedback network is shown in Fig. 1. For the following circuit, assume $\lambda = 0$ and transconductances of transistors M_1 and M_2 are g_{m1} and g_{m2} , respectively. Meanwhile, $R_1 + R_2 \gg R_{D2}$
 - (a) Please indicate which transistor will be suffered from body effect. (5%)
 - (b) What components construct the first stage of the amplifier? (5%)
 - (c) What components construct the second stage? (5%)
 - (d) What components construct the feedback network? (5%)
 - (e) What kind of feedback topology is it? (5%)
 - (f) Please derive the open-loop input impedance? (5%)
 - (g) Please derive the open-loop output impedance? (5%)
 - (h) Please derive the open-loop voltage gain? (5%)
 - (i) Please derive the closed-loop voltage gain? (5%)
 - (j) Please derive the closed-loop input impedance? (5%)
 - (k) Please derive the closed-loop output impedance? (5%)

元智大學 102 學年度研究所 碩士班 招生試題卷

系(所)別：電機工程學系碩士班

組別：電子工程組

科目：電子學

用紙第 2 頁共 2 頁

●不可使用電子計算機

 


Fig. 1

(2) (5%) Please explain the Miller's Theorem.