

# 中原大學 102 學年度 碩士班 入學考試

102/3/2 15:30 ~ 17:00 電機工程學系電子電路組

誠實是我們珍視的美德，  
我們喜愛「拒絕作弊，堅守正直」的你！

科目：電子學

(共 2 頁第 1 頁)

可使用計算機，惟僅限不具可程式及多重記憶者

不可使用計算機

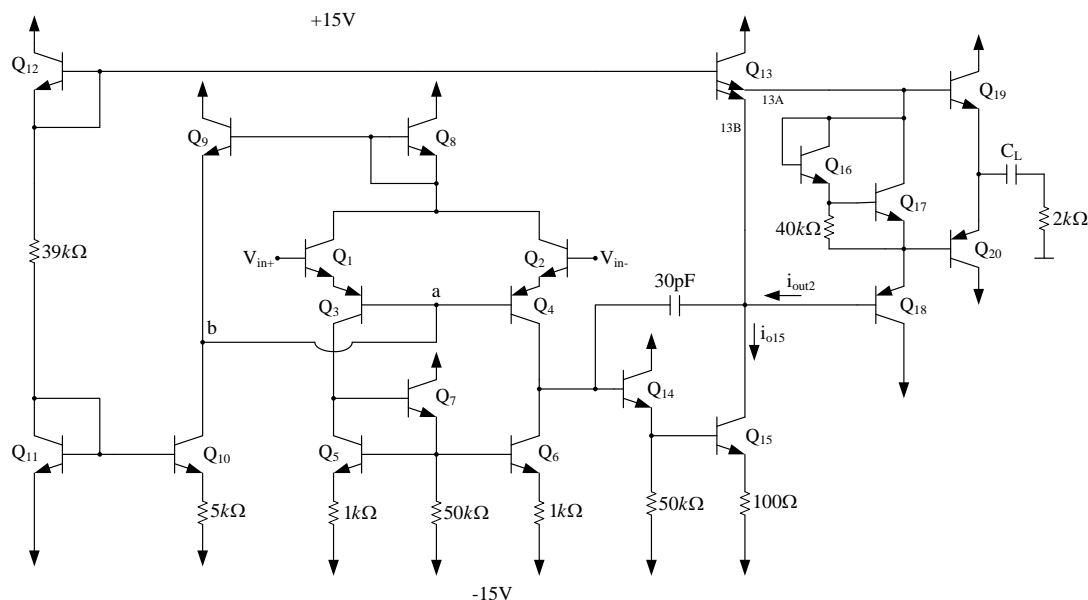


Fig. 1

- For the standard npn and pnp transistors shown in Fig. 1 the following parameters will be used:

npn:  $I_S = 10^{-14} A$ ,  $\beta = 200$ ,  $\mu = 5000$ ; pnp:  $I_S = 10^{-14} A$ ,  $\beta = 50$ ,  $\mu = 2000$ ;

except  $Q_{13}$ ,  $Q_{19}$ , and  $Q_{20}$  whose saturation currents are respectively

$I_{S13A} = 0.25 \times 10^{-14} A$ ,  $I_{S13B} = 0.75 \times 10^{-14} A$ , and  $I_{S19} = I_{S20} = 3.0 \times 10^{-14} A$ .

Referring to Fig. 1, please specify (i) the DC analysis of the output stage with the transistors  $Q_{13A}$ , and  $Q_{16}$  to  $Q_{20}$ , (10%) (ii) the small signal analysis of the output stage, (12%) (iii) the reason why the usage of the middle capacitor 30pF, (10%) (iv) the reason why the usage of  $Q_{16}$  and  $Q_{17}$  for the output response given by  $Q_{19}$  and  $Q_{20}$ , (10%) (v) the reason why the usage of the load capacitor  $C_L$ , (4%) (vi) the reason why the connection of the base and the collector of  $Q_{11}$  for a current mirror, (6%) (vii) the reason why the connected node of the two bases of the transistors  $Q_3$  and  $Q_4$  is like a grounded node, and the terminal a-b is like an open circuit, for a small signal analysis, (6%) (viii) the reason why the base of  $Q_6$  is like a grounded node when we would like to find  $R_{O6}$  from the collector of  $Q_6$ , (4%) (ix) the reason why the emitter of  $Q_4$  is in series with the  $r_{e2}$  of  $Q_2$  to the ground when we would like to find  $R_{O4}$  from the collector of  $Q_4$ , (4%) and (x) the reason why  $i_{out2} = i_{o15}$ , (4%). (70%)

2. Please (i) do the circuit analysis to find the  $V_o/(V_1-V_2)$  of the operational amplifier-based circuit shown in Fig. 2 if the three operational amplifiers are operated in active region (15%); and (ii) decide the polarities of the two input terminals of an operational amplifier shown in Fig. 2 when the three operational amplifiers are operated in active region (15%). (30%)

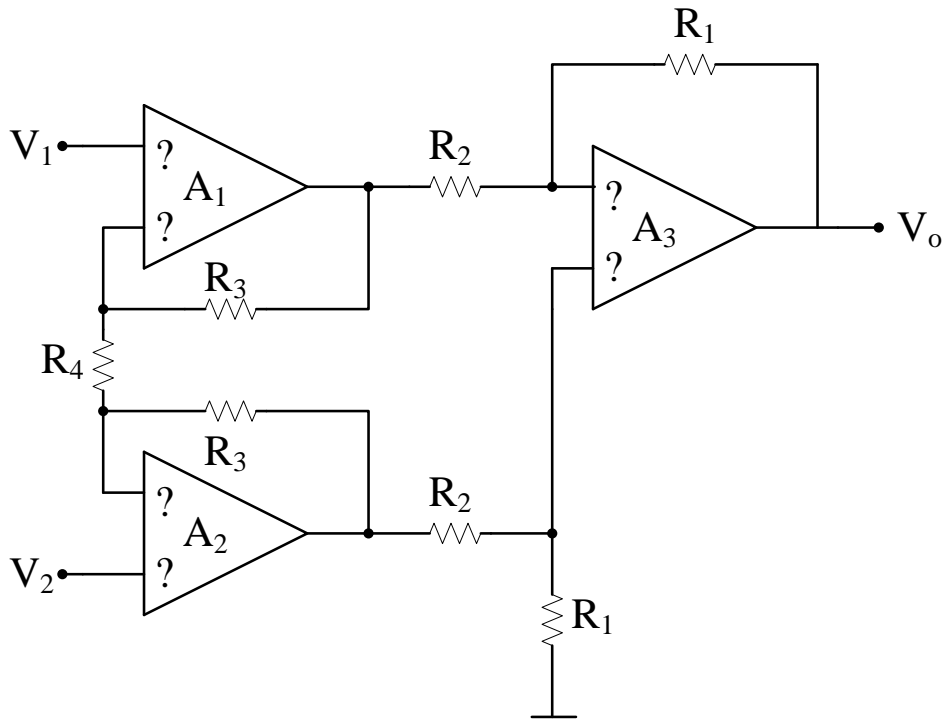


Fig. 2