

元智大學 102 學年度研究所 碩士班 招生試題卷

系(所)別： 電機工程學系碩士班 組別： 數位科技組 科目： 電子學 用紙第 | 頁共 2 頁

● 不可使用電子計算機

1. (20%) A n -channel enhance MOSFET has a drain current i_D of 9 mA at $V_{GS} = V_{DS} = 10$ V and of 1 mA at $V_{GS} = V_{DS} = 4$ V. Find (a) $k'_n(W/L)$ (10%), and (b) V_{tn} (10%) for the device.
2. (10%) Sketch a pass-transistor logic (PTL) circuit that realizes the function $Y = AC + B\bar{C}$.
3. (10%) Explain the reason why the output voltage decays for dynamic logic circuits at a very low operating frequency.
4. (55%) A two stage amplifier with feedback network is shown in Fig. 1. For the following circuit, assume $\lambda=0$ and transconductances of transistors M_1 and M_2 are g_{m1} and g_{m2} , respectively. Meanwhile, R_F is very large.
 - (a) Please indicate which transistor will be suffered from body effect. (5%)
 - (b) What components construct the first stage of the amplifier? (5%)
 - (c) What components construct the second stage? (5%)
 - (d) What components construct the feedback network? (5%)
 - (e) What kind of feedback topology is it? (5%)
 - (f) Please derive the open-loop input impedance? (5%)
 - (g) Please derive the open-loop output impedance? (5%)
 - (h) Please derive the open-loop voltage gain? (5%)
 - (i) Please derive the closed-loop voltage gain? (5%)
 - (j) Please derive the closed-loop input impedance? (5%)
 - (k) Please derive the closed-loop output impedance? (5%)

元智大學 102 學年度研究所 碩士班 招生試題卷

系(所)別： 電機工程學系碩士班 組別： 數位科技組 科目： 電子學 用紙第 一 頁共 二 頁

⊗ 不可使用電子計算機

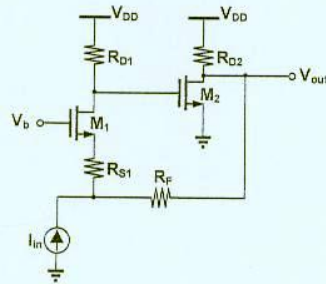


Fig. 1

5. (5%) Please derive the output impedance of the circuit shown in Fig. 2 if the transconductances of transistors Q_1 and Q_2 are g_{m1} and g_{m2} , respectively. Meanwhile, all of the transistors are with current gain of β and $V_A = \infty$

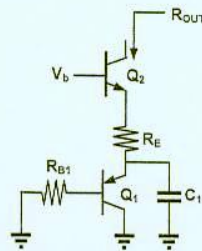


Fig. 2