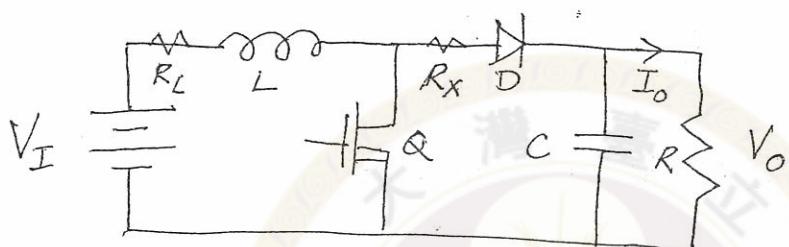


1.



- (a) Derive the voltage gain V_o/V_I in terms of transistor duty cycle for the ideal case, i.e., $R_L = R_x = 0$, Q and D are ideal. (No point given if there is no derivation) (10%)
- (b) Repeat part(a) if $R_L = R_x = 0$ but the transistor conduction voltage drop is V_Q and the diode drop is V_D (12%)
- (c) Repeat Part(a) to include the effects of V_D , V_Q , R_L and R_x (i.e. none of those is zero) (12%)

見背面

2. 如果一單相變壓器之部份數據如下：

一次側繞組匝數 $N_1 = 100$


二次側繞組匝數 $N_2 = 10$

鐵心磁阻 $R = 1$


試求一次側磁化電感 (magnetization inductance) $L_m = ?$ (13%)

3. 考慮一凸極同步發電機，其端電壓 $V_a = 1.0 \angle 0^\circ$ ，定子電流 $I_a = 1 \angle -45^\circ$ ，直軸電抗 $X_d = 1.0$ ，交軸電抗 $X_q = 0.6$ ，若忽略定子電阻值，試求開路電壓 $E_a = ?$ (以上數據均以標么值表示)。 (10%)

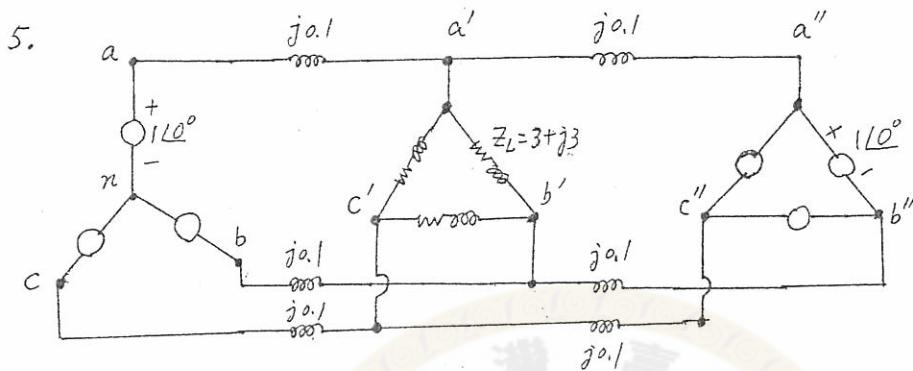
4. 考慮一部三相感應電動機，若此部電動機正由三相 60 Hz , 110 V 交流電源驅動，且滑差率 $s = 1\%$ ，試求此電動機轉子電壓之頻率為何？以 Hz 表示。 (10%)



上圖所示為一平衡三相電力系統。試求 $V_{a'b''}$ 。(10%)

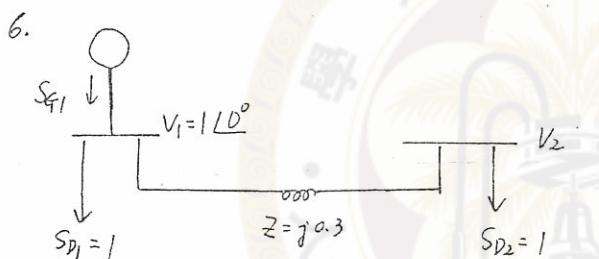

試求 V_2 。(10%)

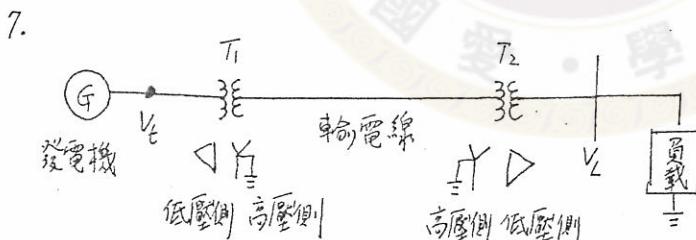

左圖所示為一平衡三相電力系統之單線圖。

各元件之額定值如下：發電機：200MVA, 20KV, X_s (同步電抗) = 0.2 pu.

T_1 ：三相變壓器，250MVA, 20/161KV, X_d (漏電抗) = 0.1 pu.

T_2 ：由三臺單相變壓器所組成，每臺單相變壓器之額定值為 75MVA, 89KV / 11KV, $X_d = 0.1$ pu。

變壓器之電阻及激磁電流可忽略不計。

輸電線：串聯電抗為 38Ω，其電阻及電容可忽略不計。

負載：定阻抗負載， $|V_L| = 11KV$, $P = 50MW$, 功率因數 0.9 落後。

選擇發電機之額定值為基準值 (BASE VALUES)，試計算發電機，變壓器 T_1 及 T_2 ，輸電線，以及負載阻抗之標幺值 (PER UNIT VALUES)，並繪出電力系統之阻抗圖 (IMPEDANCE DIAGRAM)。(13%)

試題隨卷繳回