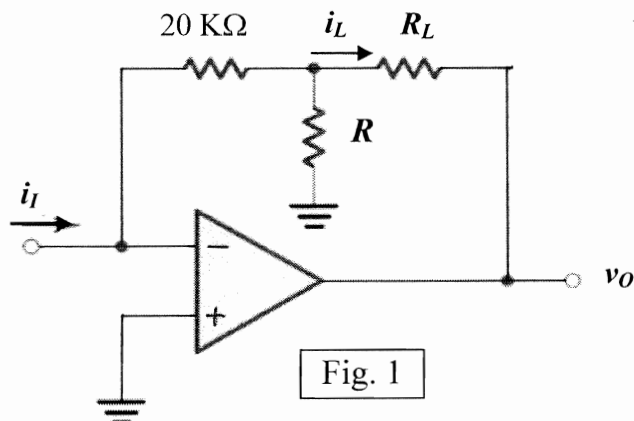


科目	電子學	適用系所	電子工程學系固態電子組	時間	100分鐘
----	-----	------	-------------	----	-------


※請務必在答案卷作答區內作答。

共 3 頁第 1 頁

- For a Si semiconductor, please briefly describe the (a) Quasi Fermi level (b) effective density of state in conduction band or valence band (c) Degenerate semiconductor (10%)
- For a PN junction, if the  $N_A \ll N_D$ , please (a) draw the minority carrier distribution in a forward bias, (b) draw the energy band diagram in the reverse bias with  $V_R$  voltage, please label the Fermi level position and the built in voltage. (10%)
- Assuming the op amp is ideal shown in Fig. 1, if we want to implant a current amplifier with a gain  $i_L/i_I = 30$ , (a) find the required value of  $R$ , (b) if  $R_L = 1 \text{ K}\Omega$ , and the op amp operates in an ideal manner that is  $v_O$  in the range  $\pm 15\text{V}$ , find the range of  $i_I$ , (c) if the amplifier is fed with a current source  $i_S = 1\text{mA}$  and source resistance of  $10 \text{ K}\Omega$ , find the  $i_L$  (12%)



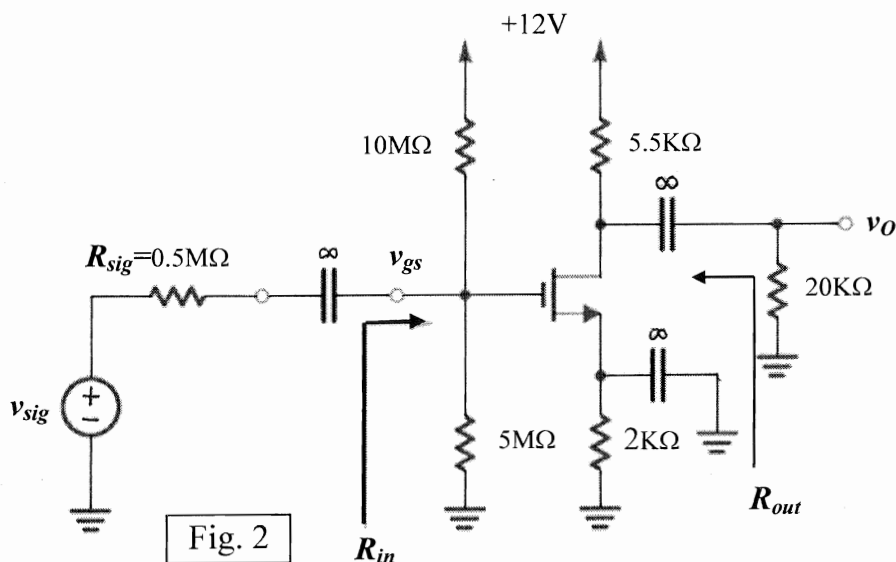- The CS stage MOS amplifier shown in Fig. 2,  $V_t = 1\text{V}$ ,  $K_n'(W/L) = 2 \text{ mA/V}^2$ ,
  - Please find the dc bias value of  $V_{GS}$  and  $I_D$  (4%)
  - if  $V_A = 50\text{V}$ , find  $g_m$  and  $r_o$  (4%)
  - Find  $R_{in}$ ,  $R_{out}$  and overall voltage gain  $G_V = v_o/v_{sig}$  (10 %)



5. Consider the circuit shown in **Fig. 3**. Let  $\beta = 100$ ,  $C_\mu = 1.5$  pF, and  $f_T = 500$  MHz for the BJT. By neglecting  $r_x$  and  $r_o$ , calculate the midband gain  $A_M$  and the 3-dB frequency  $f_H$ . (10%)

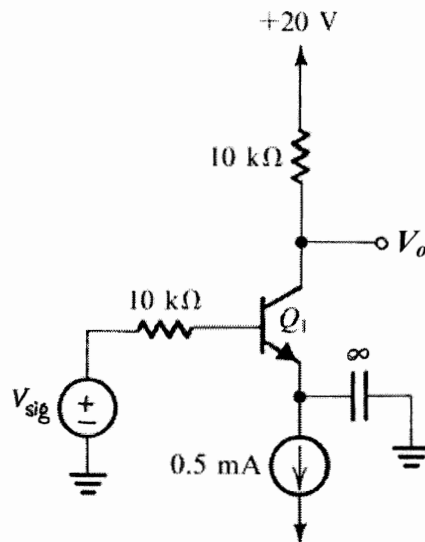


Fig. 3

6. The BJTs in the Darlington follower of **Fig. 4** have  $\beta = 100$ . If the follower is fed with a source having a  $10$  k $\Omega$  resistance and is loaded with  $1$  k $\Omega$ , find the input resistance and the output resistance. (10%)


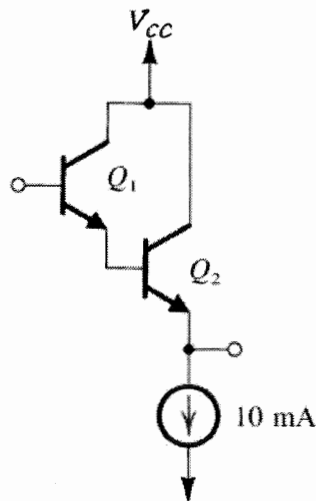


Fig. 4

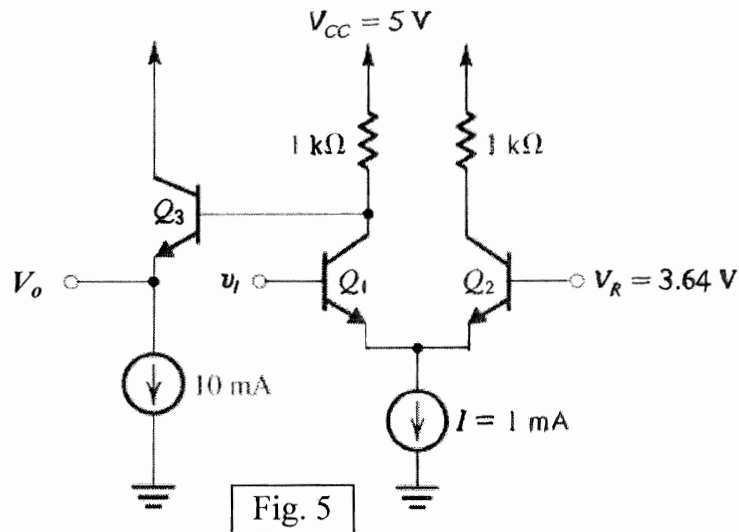7. For the differential amplifier shown in **Fig. 5**, all BJTs have  $V_{BE} = 0.7 \text{ V}$  at  $I_C = 1 \text{ mA}$  and  $\beta$  is very large. (a) If  $Q_1$  is off, determine  $v_o$ . (3%) (b) If  $Q_2$  is off, determine  $v_o$ . (3%) (c) Find  $v_i$  for  $Q_1$  conducting 99% of  $I$ . (4%) (d) Find the small-signal voltage gain. (5%)



8. The shunt-series feedback amplifier circuit shown in **Fig. 6** has  $R_D = 10 \text{ k}\Omega$ ,  $R_S = 20 \text{ k}\Omega$ , and  $R_F = 80 \text{ k}\Omega$ . Assume that  $g_{m1} = g_{m2} = 10 \text{ mA/V}$  and no body effect. (a) Find  $A_f = I_o / I_s$  and  $R_{in}$  by neglecting  $r_o$ . (10%) (b) Find  $R_{out}$  by using  $r_{o2} = 40 \text{ k}\Omega$ . (5%)

