

國立彰化師範大學 100 學年度碩士班招生考試試題

系所：機電工程學系


組別：乙組

科目：電子學


☆☆請在答案紙上作答☆☆

共 2 頁，第 1 頁

- For the circuit in Fig. 1(a), find the output voltage V_o when (1) switch off, and (2) switch on. Assume that all diodes have the same terminal characteristics ($i_D - v_D$) as shown in Fig. 1(b). (10%)
- In the circuit of Fig. 2, the diodes are ideal. Find the steady-state voltage v_{AB} . (10%)
- For the circuit in Fig. 3, find (1) the drain current I_D , (2) the input resistance R_{in} and the output resistance R_{out} , and (3) voltage gain v_o/v_s . Assume $V_t=1\text{V}$, $k'_n(W/L)=0.5 \text{ mA/V}^2$, and $V_A=\infty$. (20%)
- For the circuit of Fig. 4, the transistors have the parameters of $\beta=50$ and $V_A=\infty$, please find (1) I_1 , I_{B1} , I_{C1} , (2) g_{m1} , $r_{\pi 1}$, r_{e2} , and (3) the voltage gain v_o/v_i . Suppose that $V_{BE(\text{active})}=0.7\text{V}$. (35%)
- For the circuit of Fig. 5 with an ideal op amp, if the closed-loop voltage gain $v_O/v_I = -20\text{V/V}$, and input resistance $R_{in} = 10\text{k}\Omega$, estimate R_1 and R_2 . (10%)
- The circuit in Fig. 6 utilizes an ideal op amp. Derive (1) the voltage gain v_o/v_I , and (2) input resistance R_i . (15%)

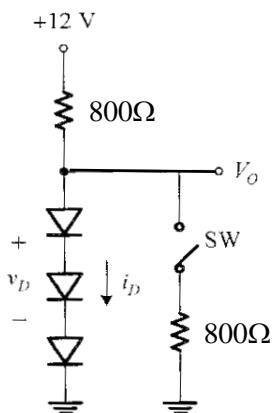

(a)

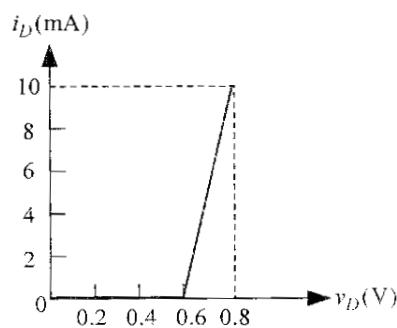

(b)

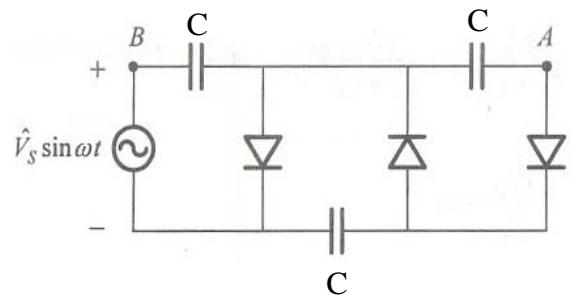


Fig. 2

Fig. 1

國立彰化師範大學 100 學年度碩士班招生考試試題

系所：機電工程學系

組別：乙組

科目：電子學

☆☆請在答案紙上作答☆☆

共 2 頁，第 2 頁

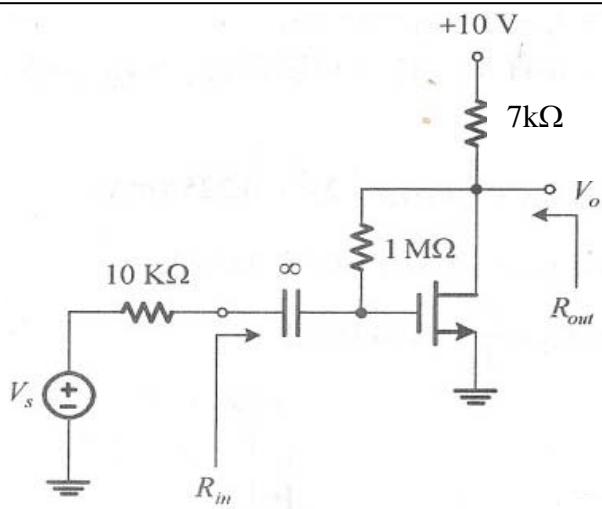


Fig. 3

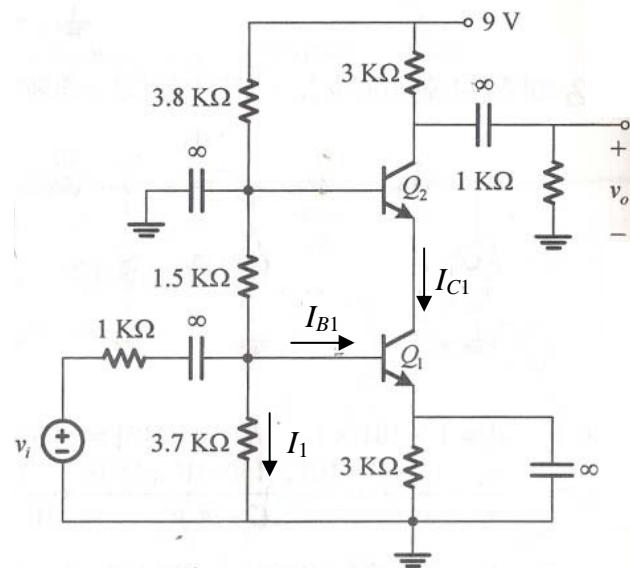


Fig. 4

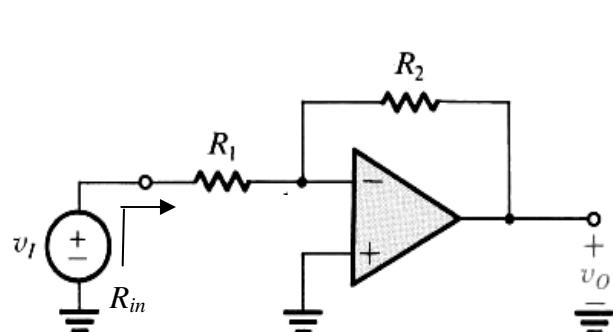


Fig. 5

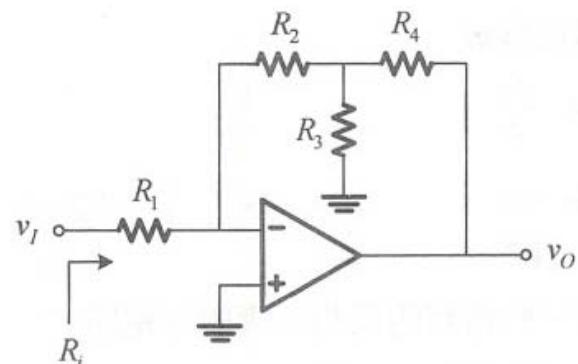


Fig. 6