



1. Assuming the op amp to be ideal, derive an expression for the closed-loop gain v_{out}/v_{in} of the circuit shown in Fig. P1. (15%)

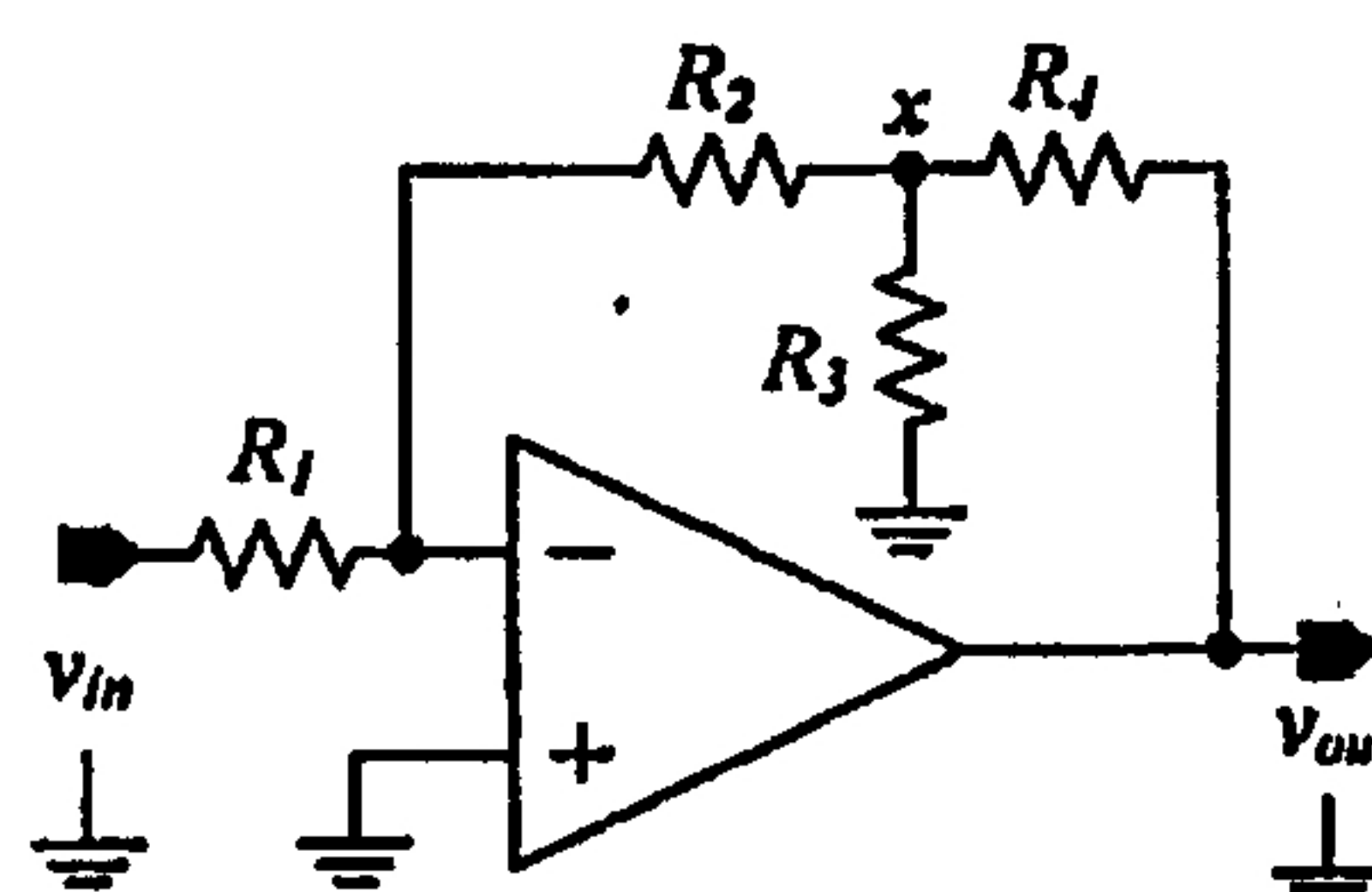


Fig. P1

2. For the circuit in Fig. P2, resistors R_1 to R_5 are set to be $2\text{ K}\Omega$.
- find the equivalent resistance to ground, R_{eq} , (5%)
 - find the equivalent resistance R_{eq} , when R_4 reduced to $1.8\text{ K}\Omega$. (10%)

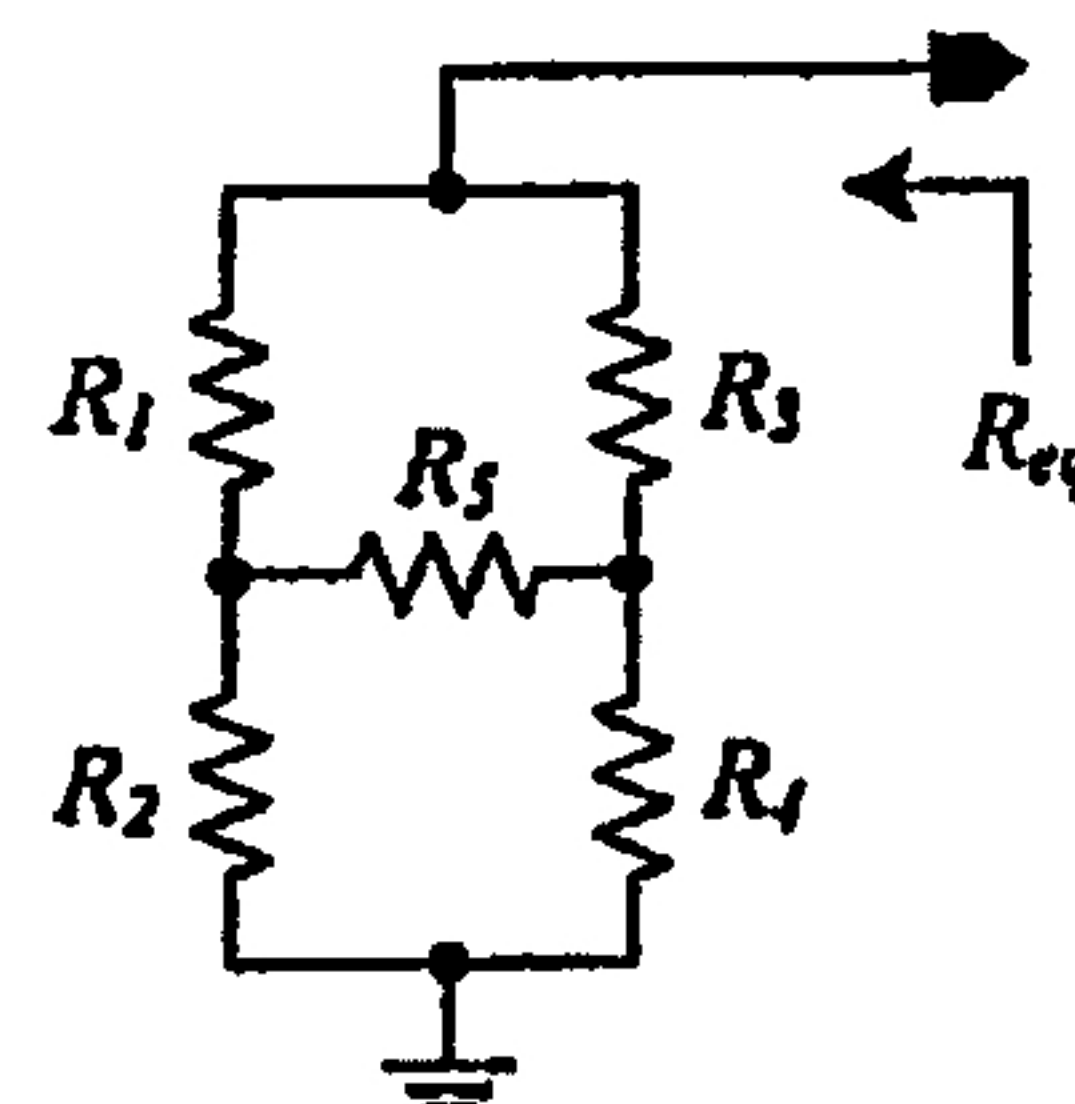


Fig. P2

3. Consider a peak rectifier fed by a 120 Hz sinusoid having a peak value $V_p = 3.3\text{ V}$. Let the load resistance $R = 100\text{ K}\Omega$. Find the value of the capacitance C that will result in a peak-to-peak ripple of 0.1 V . (20%)



4. Write down the small-signal voltage gain, Fig. P4. (10%)

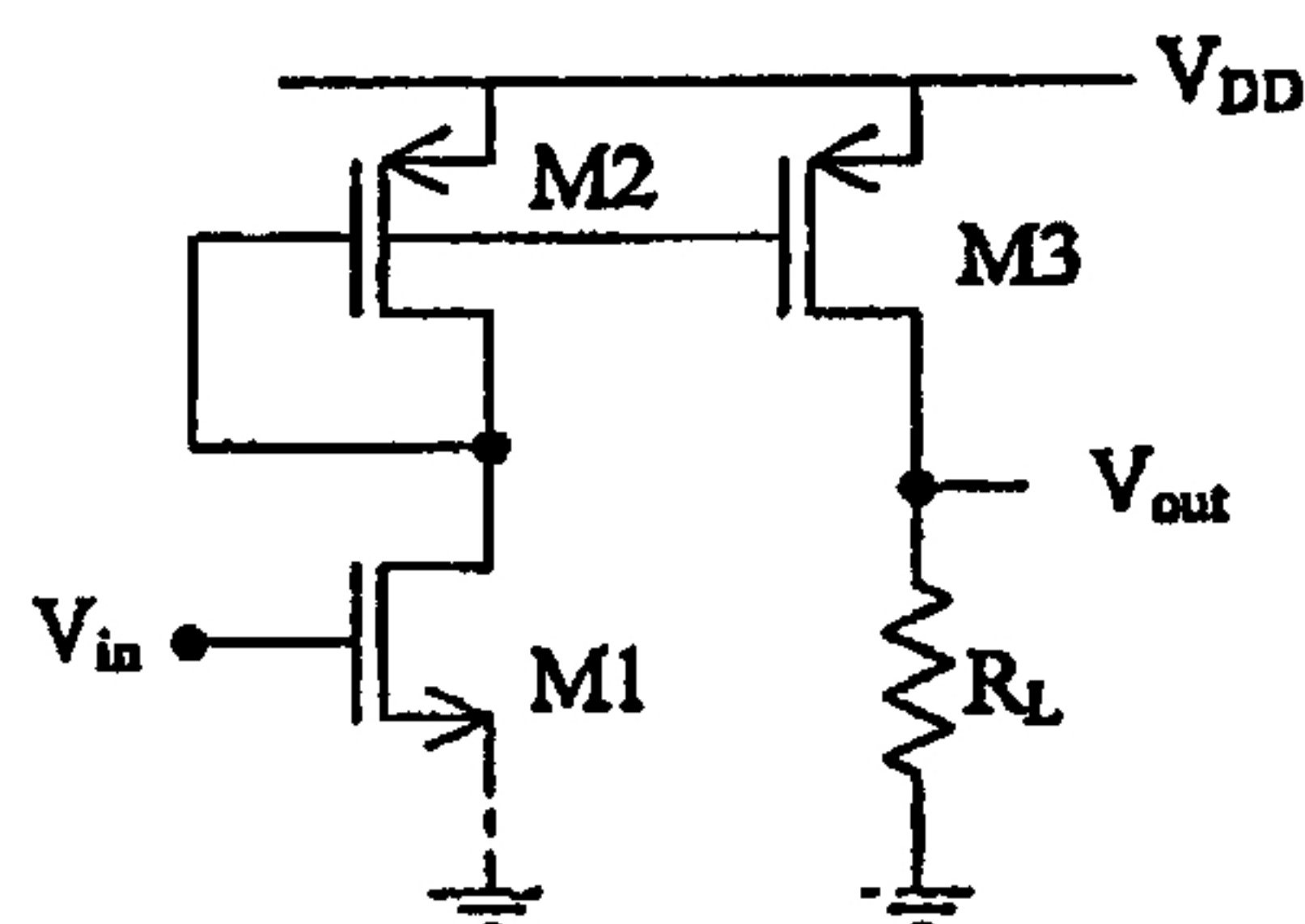


Fig. P4

5. An amplifier is shown in Fig. P5. Neglect the channel-length modulation and body effect of the transistors. The output impedance of M2 is much less than R_F . Find
- low-frequency closed-loop gain. (10%)
 - closed-loop input impedance at low frequency. (10%)

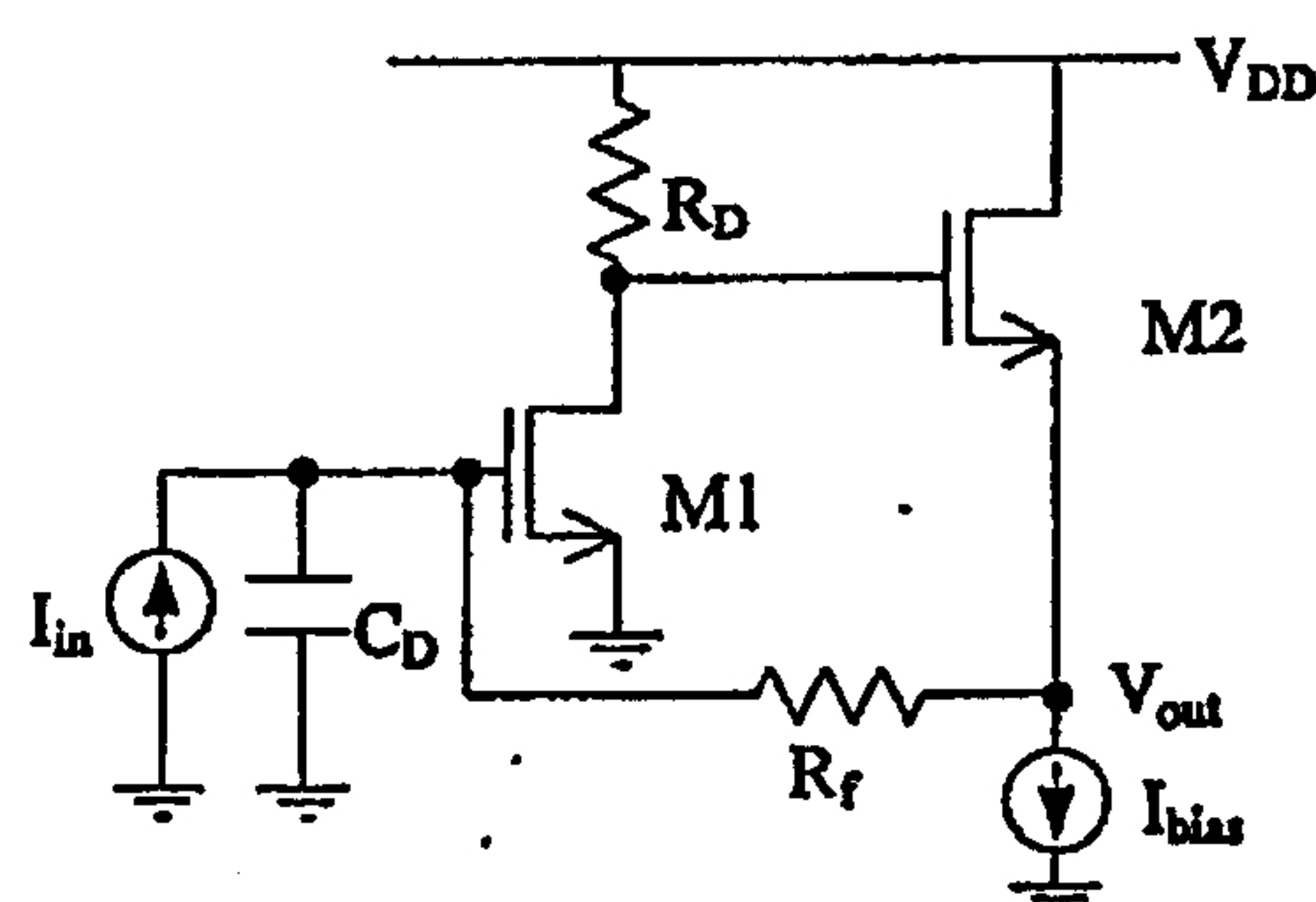


Fig. P5

6. For the circuit shown in Fig. P6, $\mu_n C_{ox} = 50 \mu\text{A}/\text{V}^2$, $\lambda = 0\text{V}^{-1}$, $(\frac{W}{L})_{M1} = 40$,

$I_{bias} = 200 \mu\text{A}$, $\gamma = 0.4\text{V}^{1/2}$, $|2\phi_F| = 0.7\text{V}$, $V_{DD} = 5\text{V}$, and $V_{t_0} = 0.6\text{V}$. λ is the

channel-length modulation coefficient. γ is the body effect coefficient.

- Calculate V_{out} for $V_{in} = 1.2\text{V}$. (10%)
- If I_{bias} is to be implemented by an NMOS transistor, find its minimum value $(\frac{W}{L})$ such that the NMOS transistor remains in saturation. (10%)

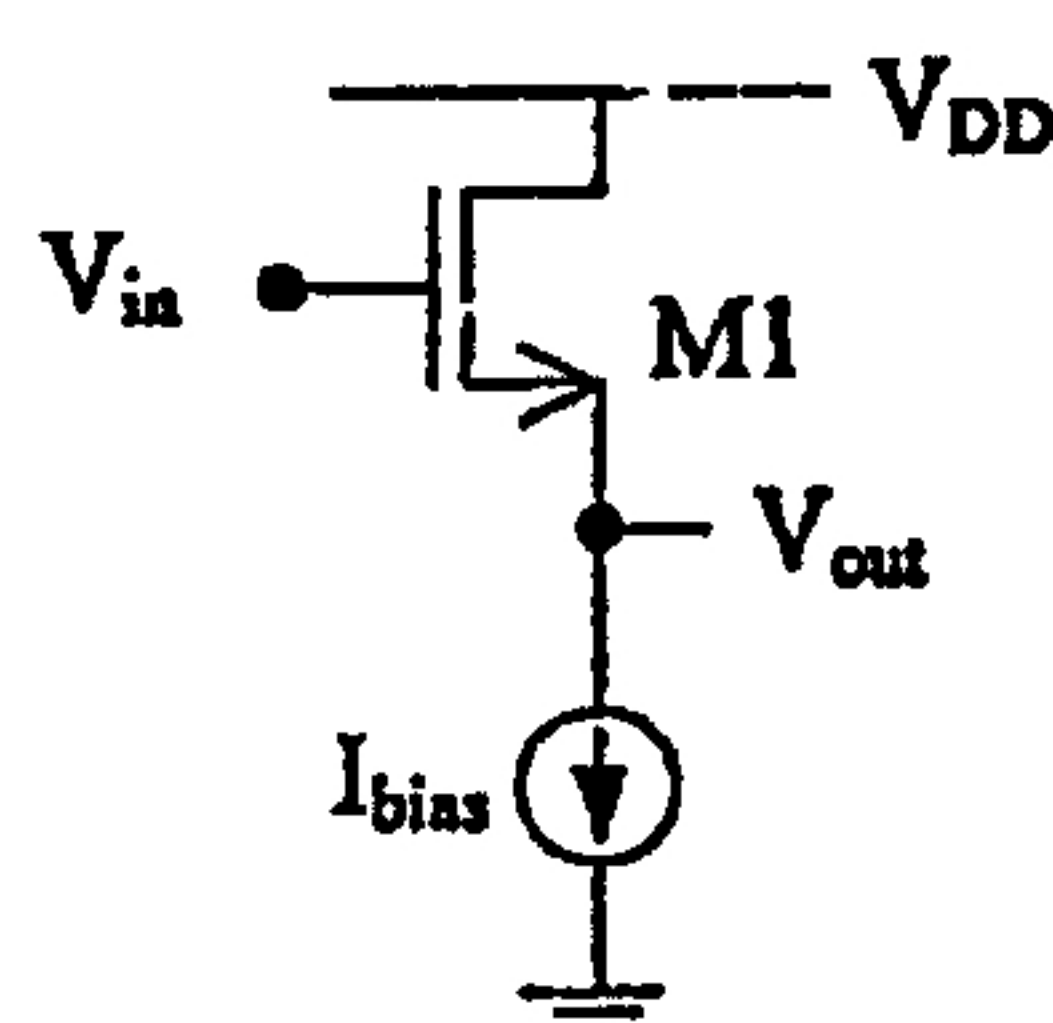


Fig. P6