



1. (20%)

Find the Thevenin equivalent of the circuit to the left of nodes A-B in Fig. 1 with $k=10$ for (a) $R_2=\infty$ and (b) $R_2=50k\Omega$.

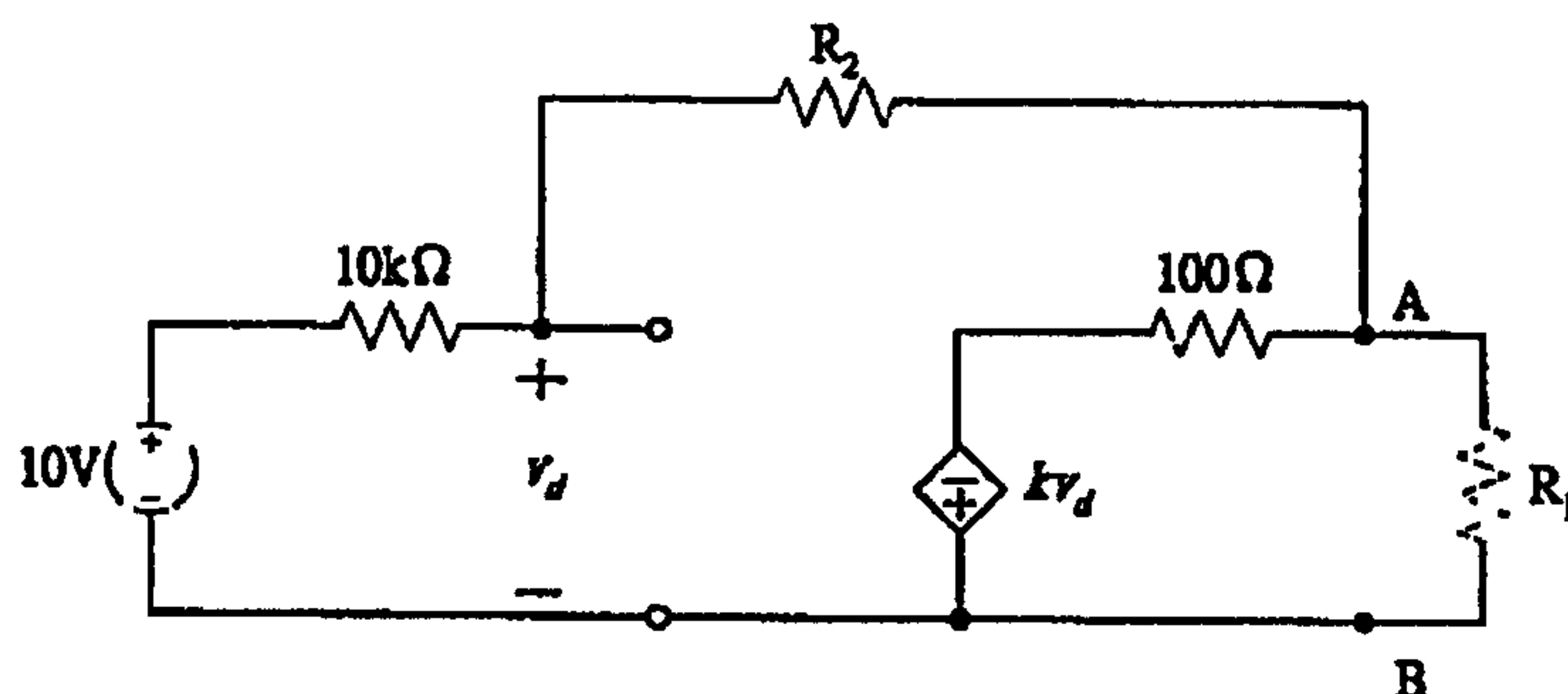


Fig. 1

2. (15%)

For the two-port network shown in Fig. 2 find the values of R_1 , R_2 , and C , given that the voltage transfer function is

$$H_v(s) = \frac{V_o(s)}{V_i(s)} = \frac{0.2}{s^2 + 3s + 2}$$

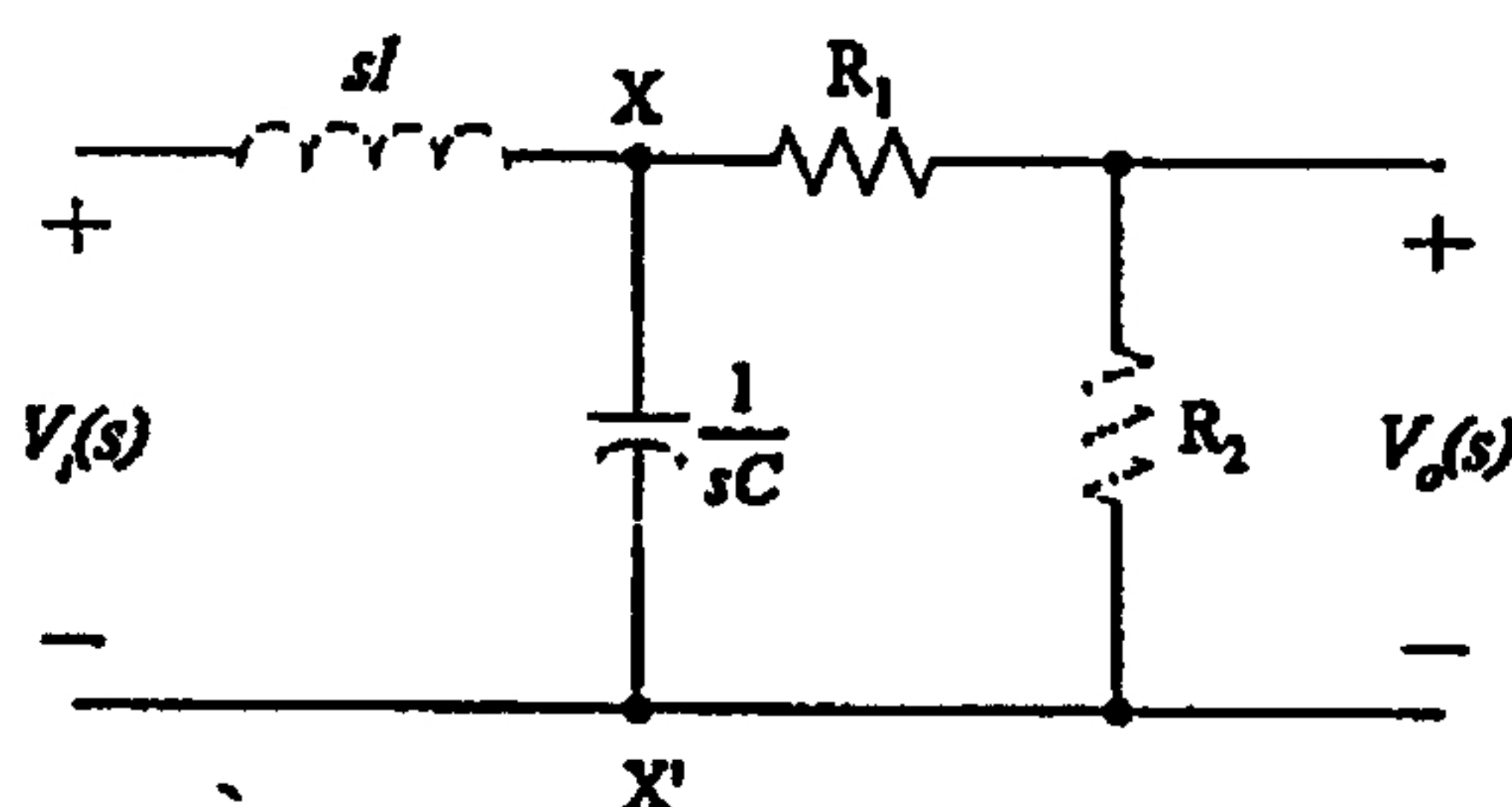


Fig. 2

3. (15%)

For the network in Fig. 3, find the value of the source voltage V which results in $V_o = 5 \angle 0^\circ \text{ V}$.

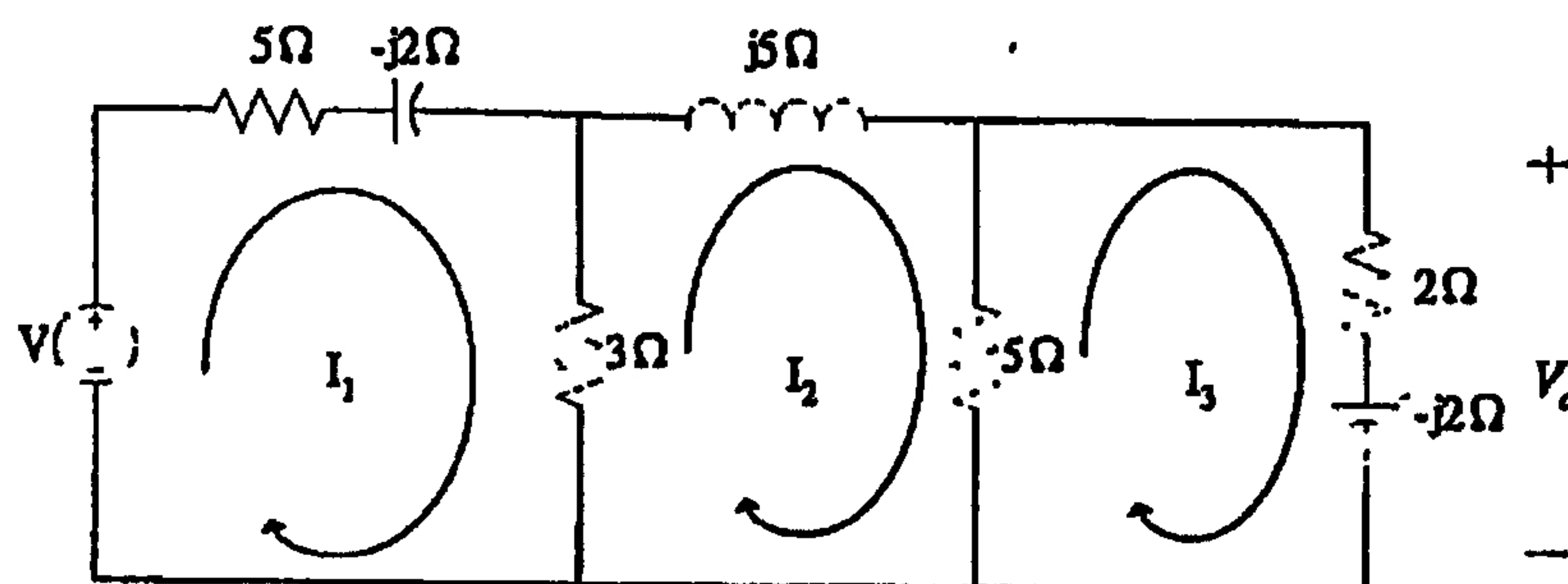


Fig. 3



4. Obtain the complete power triangle for the circuit shown in Fig.4, if the total reactive power is 2500 var (inductive). (7%) Find the branch powers P_1 and P_2 . (8%)

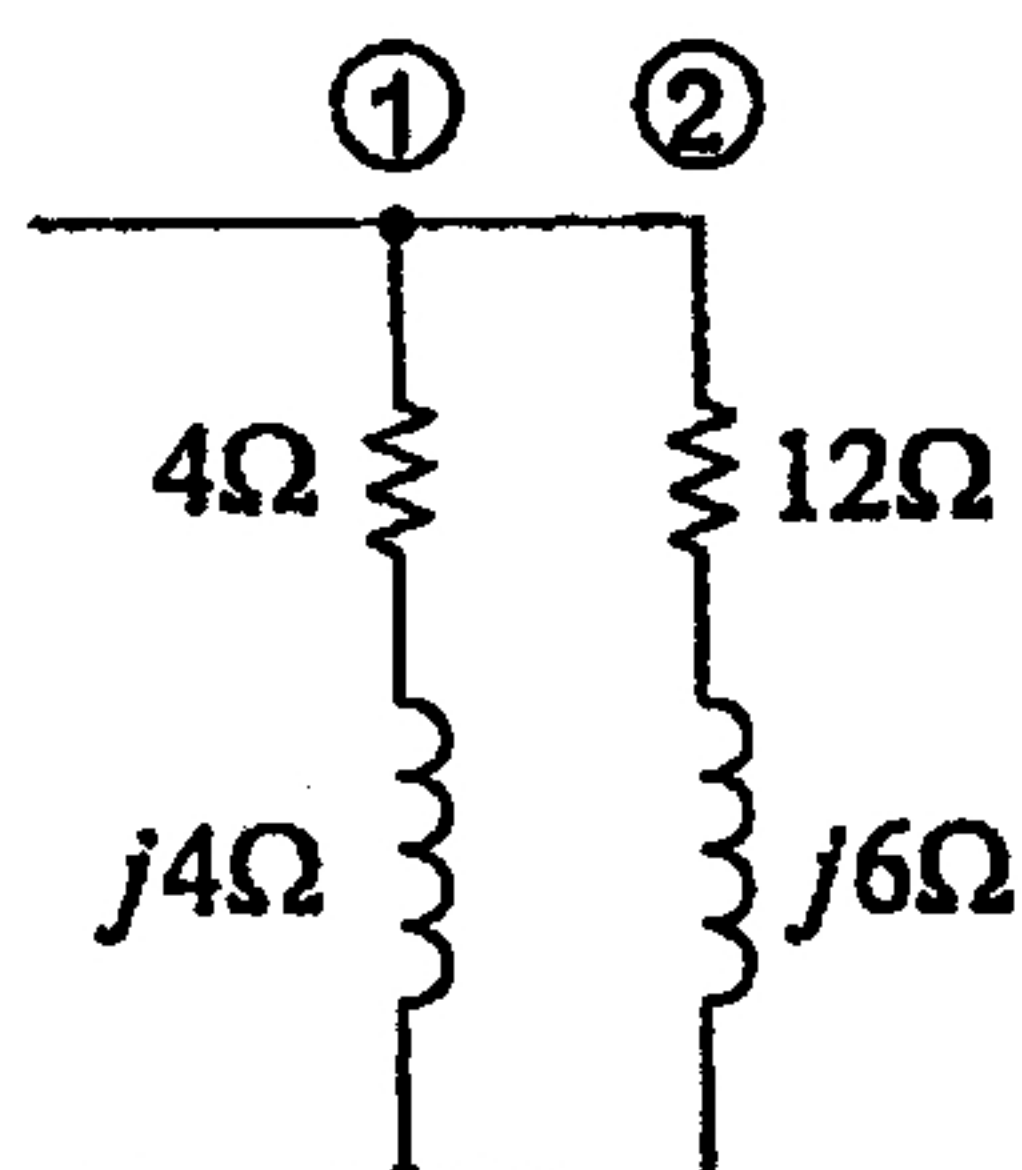


Fig.4

5. Measurements on a practical inductor at 10 MHz give $L = 8.0 \mu H$ and $Q_{\text{inductor}} = 40$. Find the ideal capacitance C for parallel resonance at 10 MHz and calculate the corresponding bandwidth β . (15%)
6. Obtain the dotted equivalent circuit for the coupled circuit shown in Fig.5 (7%), and use it to find the voltage V across the 10Ω capacitive reactance (13%).

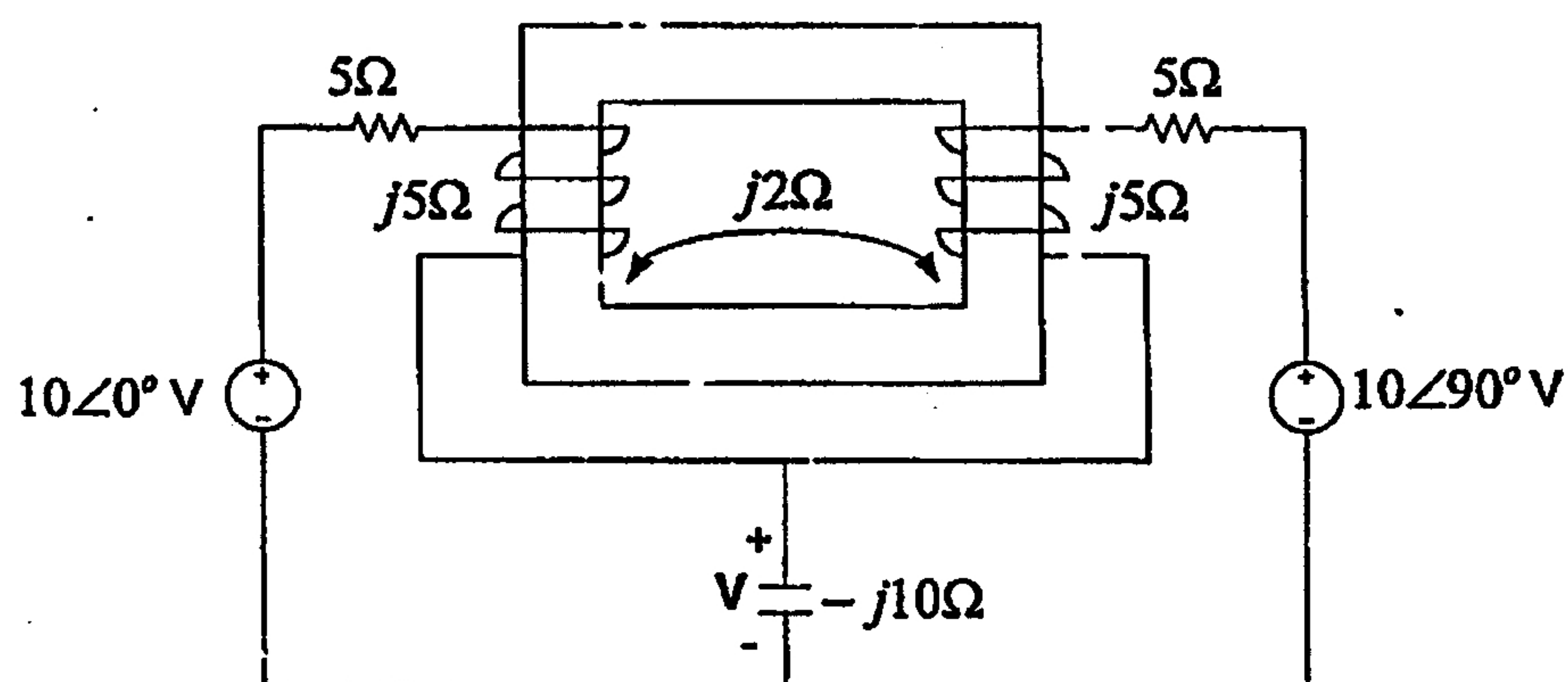


Fig.5