

國立高雄應用科技大學
九十七學年度碩士班招生考試
電子工程系（乙組）

准考證號碼 （考生必須填寫）

電子學

試題 共 2 頁，第 1 頁

注意：a. 本試題共 5 題，每題 20 分，共 100 分。

b. 作答時不必抄題。

c. 考生作答前請詳閱答案卷之考生注意事項。

1. As shown in Figure 1, $V_{CC} = 24 (V)$, $R_C = 10k\Omega$, $R_E = 270\Omega$, $\beta = 45$ for silicon transistor, $V_{CE} = 5 (V)$, $V_{BE} = 0.6 (V)$, ignore the inverses saturation current, find the value of R .

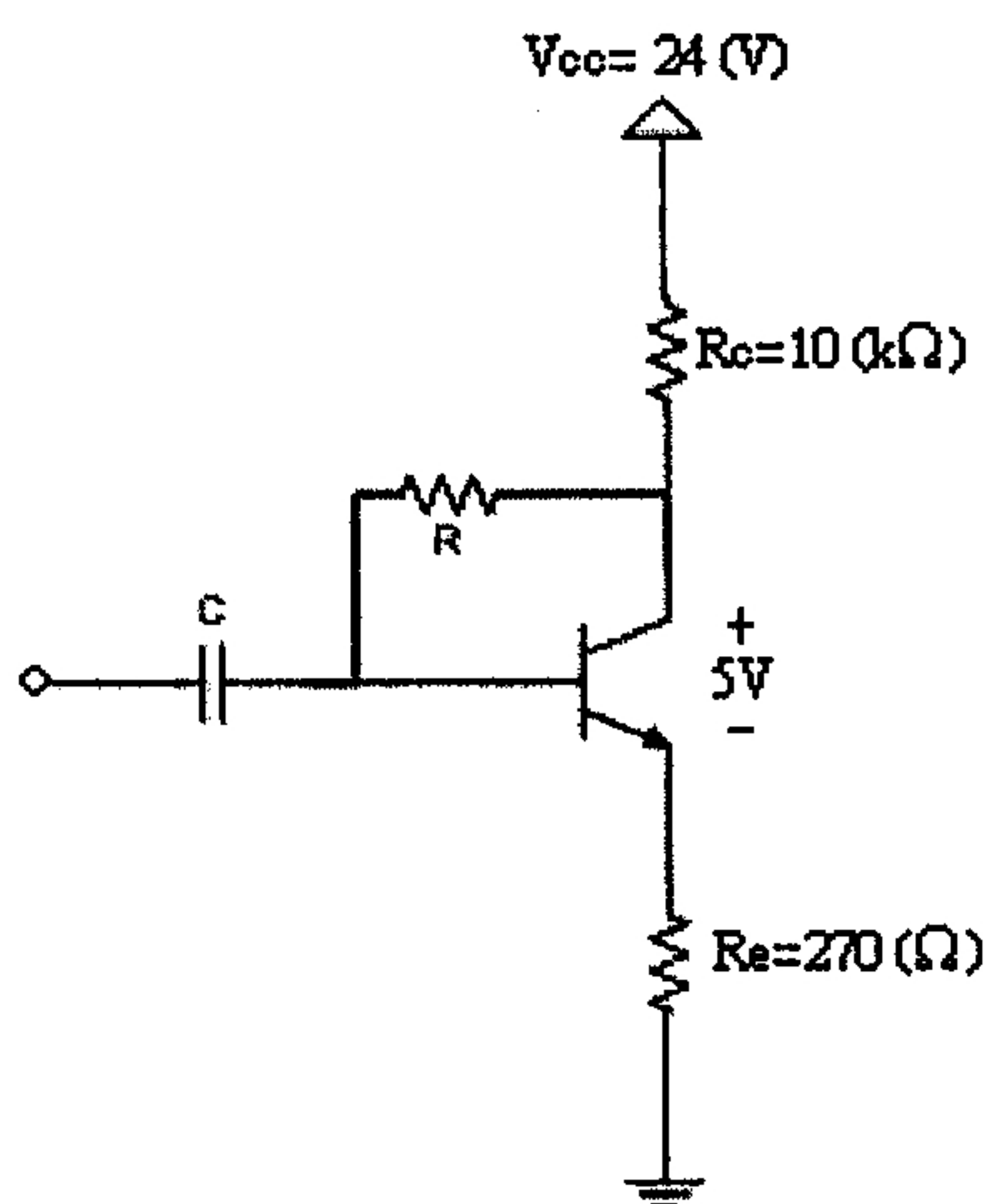


Figure 1

2. A three-pole feedback Amp has a dc gain without feedback of -10^3 . All three open-loop poles are at $f = 1MHz$.
- <a> What is the maximum value of β for which amplifier is stable?
- Assume that one of the poles is shifted to $f_1 = 200kHz$, using the value of β found in part <a>, what is the gain margin of the modified circuit?

3. As shown in figure 3, $R=2(k\Omega)$, $R_2=2(k\Omega)$, $R_1=1(k\Omega)$, $V_2=1(V)$, $V_1=0.5(V)$, find the output voltage V_o .

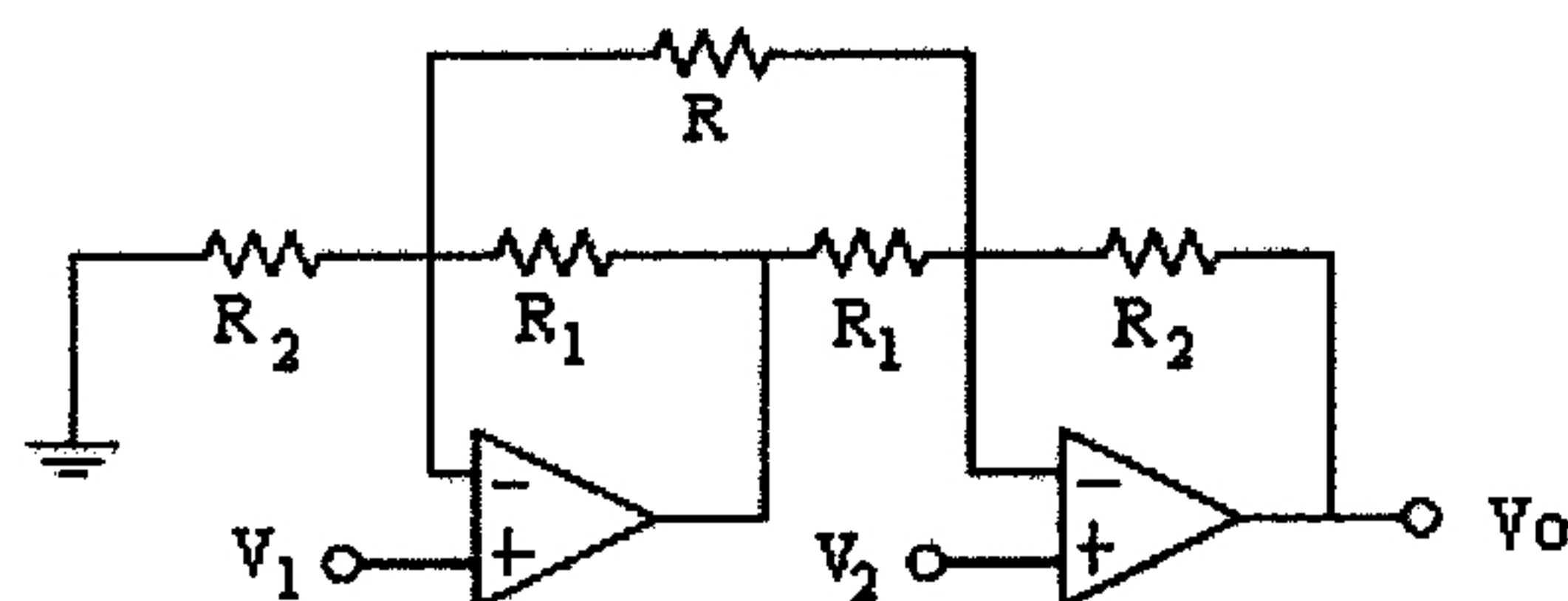


Figure 3

4. Given the Wien Bridge Oscillator in Figure 4, find the oscillating frequency and $\frac{R_1}{R_2}$.

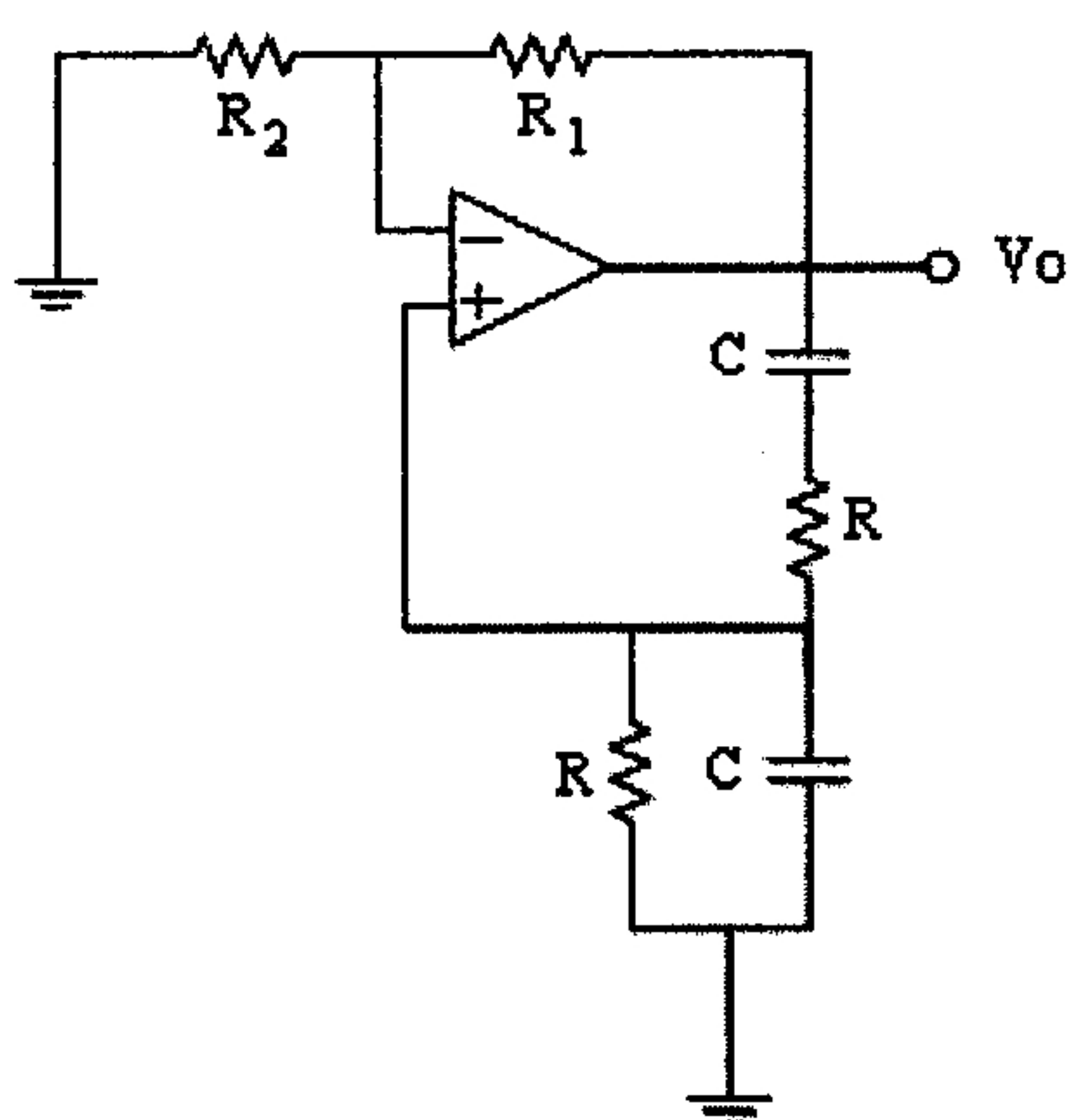


Figure 4

5. Given the circuits in Figure 5.1, Figure 5.2, and Figure 5.3, A, B, C, and D are inputs, and V_o is the output. Find the truth tables of these three circuits.

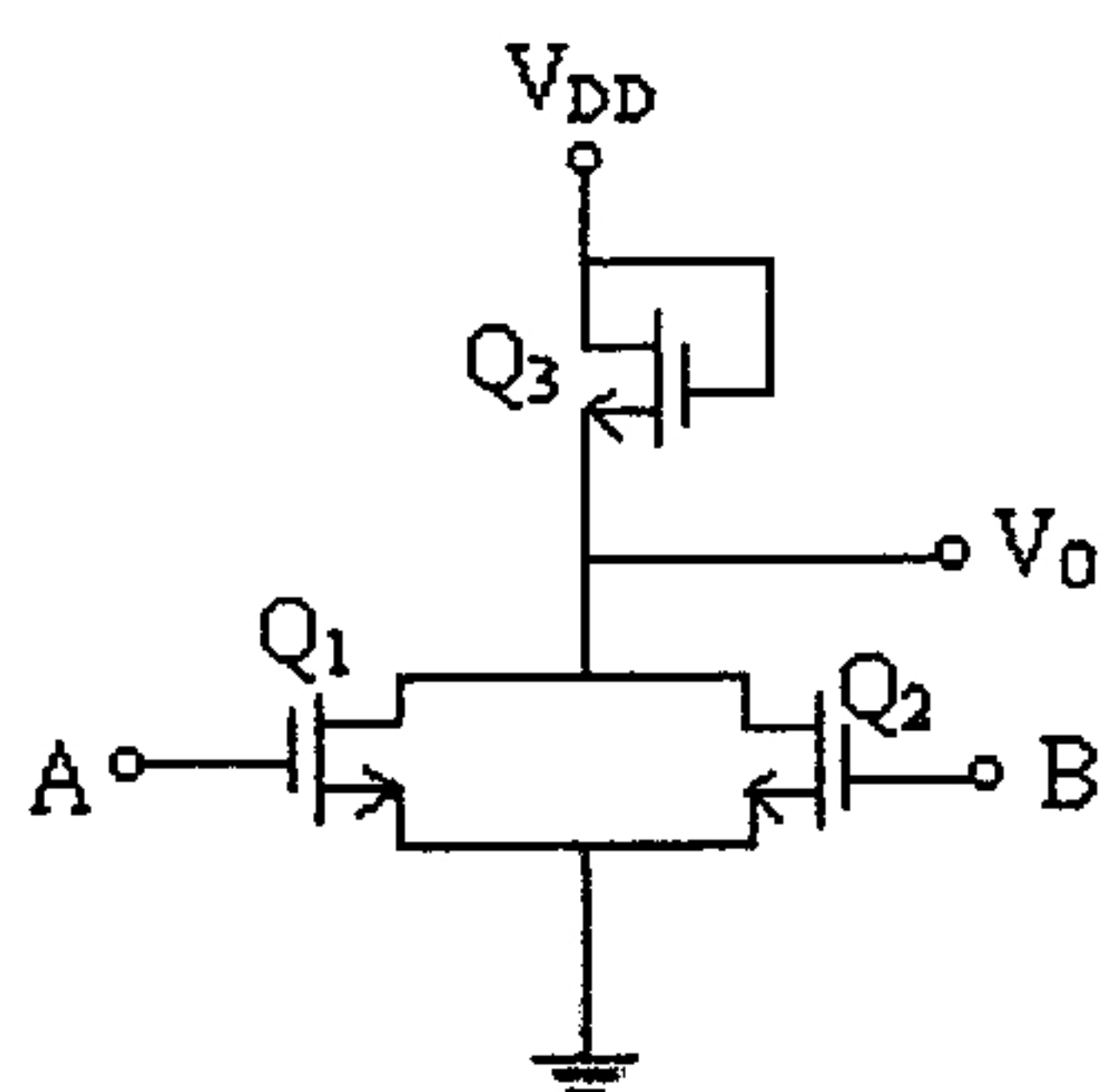


Figure 5.1

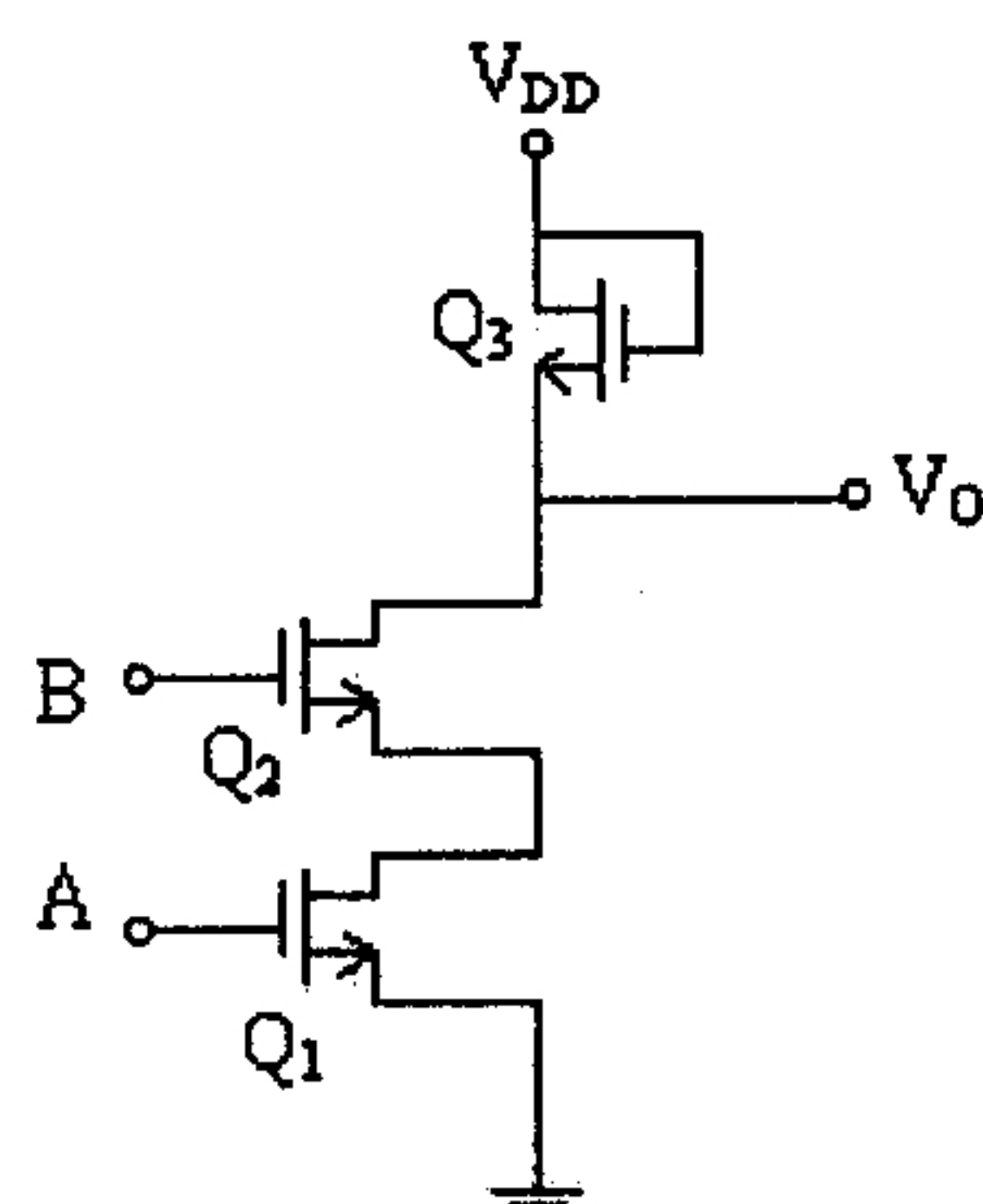


Figure 5.2

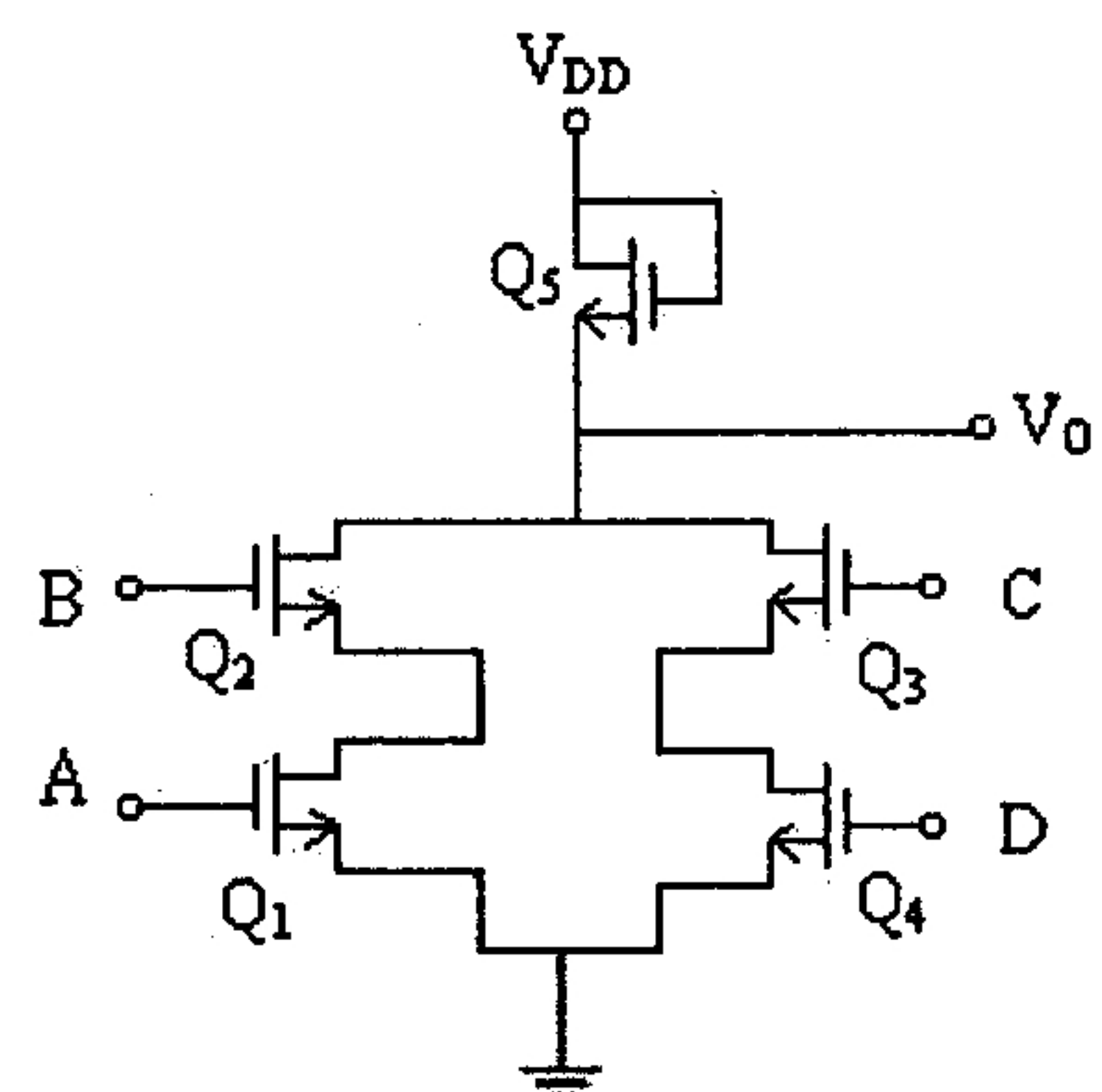


Figure 5.3