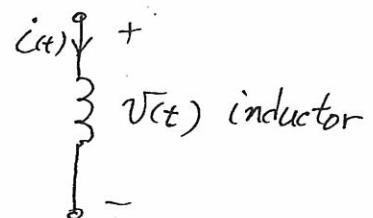


1. When the inductor voltage  $V(t)$

(8%) is positive at a particular instant,

what's the sign of the current  $i(t)$ ?


Is it positive or negative? Explain why.



2. (a) What's the average diode current  $i_d$ ?

(8%)

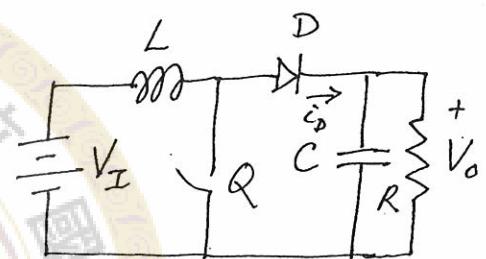(b) Check the mode of operation, continuous mode or discontinuous mode?




$$V_I = 100V, L = 100\mu H, R = 10\Omega, C \text{ very large}, V_o = 40V$$

ideal switches,  $f_s = 100\text{ KHz}$

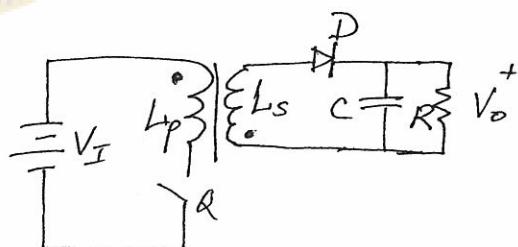3.

(6%) (a). What's the peak current of Transistor Q?



(5%) (b). What's the peak voltage of Q?

$$V_I = 100V, V_o = 50V, L_p = 400\mu H$$

$$L_s = 100\mu H, \text{ ideal switches, } C \text{ very large, } f_s = 100\text{ KHz and } R = 5\Omega,$$


見背面

4. Explain the principle of the production of a rotating magnetic field by means of 3-phase windings. (10 分)

5. The rotor of a six-pole synchronous generator is rotating at a mechanical speed of 1200 rpm (rotation per minute). What is the frequency of the generated voltage in Hz (hertz)? (10 分)

6. Draw the torque-slip curve for induction motors. (13 分)

7.

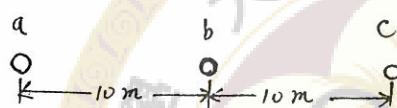


左圖所示為一三相，161KV, 60Hz 之輸電線，假設  $i_a + i_b + i_c = 0$ ，每相導線之半徑  $r = 1\text{cm}$ 。

(a) 當三相線路未換位 (UNTRANSPOSED) 時， $\begin{bmatrix} \lambda_a \\ \lambda_b \\ \lambda_c \end{bmatrix} = L_{abc} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix}$ ，試求電感矩陣  $L_{abc}$ 。 (6%)


(b) 將三相線路完全換位 (COMPLETELY TRANSPOSED)，以便將  $L_{abc}$  變成一個 DIAGONAL MATRIX  $L_{abc}'$ ，試求  $L_{abc}'$ 。 (6%)

8.

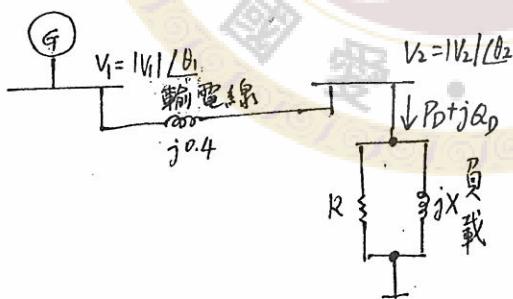

假設  $|V_1|$  固定為 1.03，負載之  $\frac{R}{X}$  固定為 0.25，輸電線之電阻及電容可忽略不計。試求  $P_0$  之最大值。 (11%)

9.

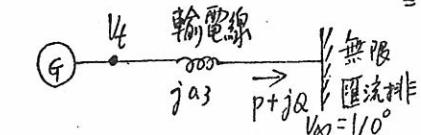

有一圓極同步發電機，其同步電抗  $X_S = 0.7$ ，電極電阻可忽略不計，

發電機端電壓  $V_f$  之大小為  $|V_f| = 1.03$ 。此發電機經由一輸電線供電給無限匯流排，假設輸電線之串聯電抗為 0.3，電阻及電容可忽略不計。無限匯流排之電壓  $V_{oo} = 1∠0^\circ$ ，有效電力  $P = 1$ 。試求同步發電機之開路電壓 (OPEN-CIRCUIT VOLTAGE)。 (10%)