 



- (7%) What is harmonic distortion? What causes it?
- (8%) What is the CMRR? For what types of application is it important?

- (15%) Consider the half-wave rectifier circuit shown on the right. Let  $v_s$  be a sinusoid with 10-V peak amplitude, and let  $R = 1\text{ k}\Omega$ . Use the constant-voltage-drop diode model with  $V_D = 0.7\text{ V}$ .
  - Sketch the transfer characteristic.
  - Sketch the waveform of  $v_o$ .
  - Find the average value of  $v_o$ .
  - Find the peak current in the diode.
  - Find the PIV of the diode.



- (15%) Suppose we have an NMOS transistor that has  $g_m = 2\text{ mS}$  and  $r_d = 5\text{ k}\Omega$  for a  $Q$  point of  $V_{GSQ} = 2\text{ V}$ ,  $I_{DQ} = 4\text{ mA}$ , and  $V_{DSQ} = 10\text{ V}$ . Sketch the drain characteristics to scale for a small region around the  $Q$  point, say, for  $v_{GS} = 1.8, 2.0, 2.2\text{ V}$  and for  $9.0 < v_{DS} < 11.0\text{ V}$ .

 - (15%) For the constant-current source circuit shown on the right, find the collector current  $I$  and the output resistance. The BJT is specified to have  $\beta = 100$ ,  $V_{BE} = 0.7\text{ V}$ , and  $V_A = 100\text{ V}$ . If the collector voltage undergoes a change of  $10\text{ V}$  while the BJT remains in the active mode, what is the corresponding change in collector current?



- (20%) An op amp with bandwidth  $f_t = 20\text{ MHz}$ , slew rate  $SR = 10\text{ V}/\mu\text{s}$ , and output saturation  $V_{o\text{max}} = 10\text{ V}$  is used in the design of a noninverting amplifier. The nominal gain of the noninverting amplifier is 10. Assume a sine-wave input with peak amplitude  $V_i$ .
  - If  $V_i = 0.5\text{ V}$ , what is the maximum frequency before the output distorts?
  - If  $f = 200\text{ kHz}$ , what is the maximum value of  $V_i$  before the output distorts?
  - If  $V_i = 50\text{ mV}$ , what is the useful frequency range of operation?
  - If  $f = 50\text{ kHz}$ , what is the useful input voltage range?
- (20%) There is a three-input CMOS NAND gate.
  - Draw the circuit diagram of the NAND gate.
  - Draw its equivalent circuit (open and closed switches) if all inputs are high.
  - Redraw (b) if all inputs are low.